

9.1 A sinusoidal voltage is given by the expression

$$v = 100 \cos(240\pi t + 45^\circ) \text{ mV.}$$

Find (a) f in hertz; (b) T in milliseconds; (c) V_m ; (d) $v(0)$; (e) ϕ in degrees and radians; (f) the smallest positive value of t at which $v = 0$; and (g) the smallest positive value of t at which $dv/dt = 0$.

Solution :

$$[\mathbf{a}] \quad \omega = 2\pi f = 240\pi \text{ rad/s}, \quad f = \frac{\omega}{2\pi} = 120 \text{ Hz}$$

$$[\mathbf{b}] \quad T = 1/f = 8.33 \text{ ms}$$

$$[\mathbf{c}] \quad V_m = 100 \text{ V}$$

$$[\mathbf{d}] \quad v(0) = 100 \cos(45^\circ) = 70.71 \text{ V}$$

$$[\mathbf{e}] \quad \phi = 45^\circ; \quad \phi = \frac{45^\circ(2\pi)}{360^\circ} = \frac{\pi}{4} = 0.7854 \text{ rad}$$

$$[\mathbf{f}] \quad V = 0 \text{ when } 240\pi t + 45^\circ = 90^\circ. \text{ Now resolve the units:}$$

$$(240\pi \text{ rad/s})t = \frac{45^\circ}{57.3^\circ/\text{rad}} = \frac{\pi}{4} \text{ rad}, \quad t = 1.042 \text{ ms}$$

$$[\mathbf{g}] \quad (dv/dt) = (-100)240\pi \sin(240\pi t + 45^\circ)$$

$$(dv/dt) = 0 \quad \text{when} \quad 240\pi t + 45^\circ = 180^\circ$$


$$\text{or} \quad 240\pi t = \frac{135^\circ}{57.3^\circ/\text{rad}} = \frac{3\pi}{4} \text{ rad}$$

$$\text{Therefore} \quad t = 3.125 \text{ ms}$$

9.2 In a single graph, sketch $v = 60 \cos(\omega t + \phi)$ versus ωt for $\phi = -60^\circ, -30^\circ, 0^\circ, 30^\circ, \text{ and } 60^\circ$.

- State whether the voltage function is shifting to the right or left as ϕ becomes more positive.
- What is the direction of shift if ϕ changes from 0 to -30° ?

Solution :

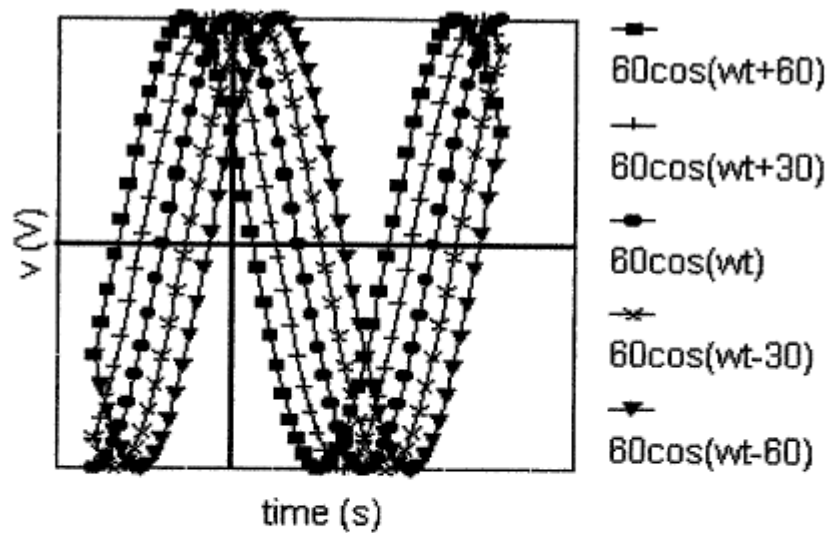

[a] Left as ϕ becomes more positive

[b] Right

9.3 At $t = -250/6 \mu\text{s}$, a sinusoidal voltage is known to be zero and going positive. The voltage is next zero at $t = 1250/6 \mu\text{s}$. It is also known that the voltage is 75 V at $t = 0$.

a) What is the frequency of v in hertz?

b) What is the expression for v ?

Solution:

$$[\text{a}] \quad \frac{T}{2} = \frac{1250}{6} + \frac{250}{6} = 250 \mu\text{s}; \quad T = 500 \mu\text{s}$$

$$f = \frac{1}{T} = \frac{10^6}{500} = 2000 \text{ Hz}$$

$$[\text{b}] \quad v = V_m \sin(\omega t + \theta)$$

$$\omega = 2\pi f = 4000\pi \text{ rad/s}$$

$$4000\pi \left(\frac{-250}{6} \times 10^{-6} \right) + \theta = 0; \quad \therefore \theta = \frac{\pi}{6} \text{ rad} = 30^\circ$$

$$v = V_m \sin[4000\pi t + 30^\circ]$$

$$75 = V_m \sin 30^\circ; \quad V_m = 150 \text{ V}$$

$$v = 150 \sin[4000\pi t + 30^\circ] = 150 \cos[4000\pi t - 60^\circ] \text{ V}$$

9.4 A sinusoidal current is zero at $t = 150 \mu\text{s}$ and increasing at a rate of $2 \times 10^4 \pi \text{ A/s}$. The maximum amplitude of the voltage is 10 A.

- a) What is the frequency of v in radians per second?
- b) What is the expression for v ?

Solution:

[a] By hypothesis

$$i = 10 \cos(\omega t + \theta)$$

$$\frac{di}{dt} = -10\omega \sin(\omega t + \theta)$$

$$\therefore 10\omega = 20,000\pi; \quad \omega = 2000\pi \text{ rad/s}$$

$$[\text{b}] \quad f = \frac{\omega}{2\pi} = 1000 \text{ Hz}; \quad T = \frac{1}{f} = 1 \text{ ms} = 1000 \mu\text{s}$$

$$\frac{150}{1000} = \frac{3}{20}, \quad \therefore \theta = -90 - \frac{3}{20}(360) = -144^\circ$$

$$\therefore i = 10 \cos(2000\pi t - 144^\circ) \text{ A}$$

9.5 Consider the sinusoidal voltage

$$v(t) = 170 \cos(120\pi t - 60^\circ) \text{ V.}$$

- a) What is the maximum amplitude of the voltage?
- b) What is the frequency in hertz?
- c) What is the frequency in radians per second?
- d) What is the phase angle in radians?
- e) What is the phase angle in degrees?
- f) What is the period in milliseconds?
- g) What is the first time after $t = 0$ that $v = 170 \text{ V}$?
- h) The sinusoidal function is shifted $125/18 \text{ ms}$ to the right along the time axis. What is the expression for $v(t)$?
- i) What is the minimum number of milliseconds that the function must be shifted to the right if the expression for $v(t)$ is $170 \sin 120\pi t \text{ V}$?
- j) What is the minimum number of milliseconds that the function must be shifted to the left if the expression for $v(t)$ is $170 \cos 120\pi t \text{ V}$?

Solution:

[a] 170 V

[b] $2\pi f = 120\pi; \quad f = 60 \text{ Hz}$

[c] $\omega = 120\pi = 376.99 \text{ rad/s}$

[d] $\theta(\text{rad}) = \frac{-\pi}{180}(60) = \frac{-\pi}{3} = -1.05 \text{ rad}$

[e] $\theta = -60^\circ$

[f] $T = \frac{1}{f} = \frac{1}{60} = 16.67 \text{ ms}$

[g] $120\pi t - \frac{\pi}{3} = 0; \quad \therefore t = \frac{1}{360} = 2.78 \text{ ms}$

[h]
$$\begin{aligned} v &= 170 \cos \left[120\pi \left(t + \frac{0.125}{18} \right) - \frac{\pi}{3} \right] \\ &= 170 \cos [120\pi t + (15\pi/18) - (\pi/3)] \\ &= 170 \cos [120\pi t + (\pi/2)] \\ &= -170 \sin 120\pi t \text{ V} \end{aligned}$$

[i] $120\pi(t - t_o) - (\pi/3) = 120\pi t - (\pi/2)$

$$\therefore 120\pi t_o = \frac{\pi}{6}; \quad t_o = \frac{25}{18} \text{ ms}$$

[j] $120\pi(t - t_o) - (\pi/3) = 120\pi t$

$$\therefore 120\pi t_o = \frac{\pi}{3}; \quad t_o = \frac{25}{9} \text{ ms}$$

9.6 Show that

$$\int_{t_0}^{t_0+T} V_m^2 \cos^2(\omega t + \phi) dt = \frac{V_m^2 T}{2}$$

Solution:

$$\begin{aligned} u &= \int_{t_0}^{t_0+T} V_m^2 \cos^2(\omega t + \phi) dt \\ &= V_m^2 \int_{t_0}^{t_0+T} \frac{1}{2} + \frac{1}{2} \cos(2\omega t + 2\phi) dt \\ &= \frac{V_m^2}{2} \left\{ \int_{t_0}^{t_0+T} dt + \int_{t_0}^{t_0+T} \cos(2\omega t + 2\phi) dt \right\} \\ &= \frac{V_m^2}{2} \left\{ T + \frac{1}{2\omega} [\sin(2\omega t + 2\phi)]_{t_0}^{t_0+T} \right\} \\ &= \frac{V_m^2}{2} \left\{ T + \frac{1}{2\omega} [\sin(2\omega t_0 + 4\pi + 2\phi) - \sin(2\omega t_0 + 2\phi)] \right\} \\ &= V_m^2 \left(\frac{T}{2} \right) + \frac{1}{2\omega} (0) = V_m^2 \left(\frac{T}{2} \right) \end{aligned}$$


9.7 The rms value of the sinusoidal voltage supplied to the convenience outlet of a U.S. home is 120 V. What is the maximum value of the voltage at the outlet?

Solution

$$V_m = \sqrt{2} V_{\text{rms}} = \sqrt{2}(120) = 169.71 \text{ V}$$

9.8 Find the rms value of the half-wave rectified sinusoidal voltage shown.

Figure P9.8

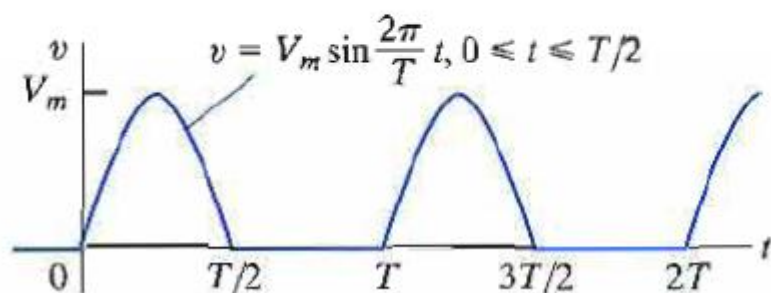

Solution:

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^{T/2} V_m^2 \sin^2 \frac{2\pi}{T} t dt}$$

$$\int_0^{T/2} V_m^2 \sin^2 \left(\frac{2\pi}{T} t \right) dt = \frac{V_m^2}{2} \int_0^{T/2} \left(1 - \cos \frac{4\pi}{T} t \right) dt = \frac{V_m^2 T}{4}$$

$$\text{Therefore } V_{\text{rms}} = \sqrt{\frac{1}{T} \frac{V_m^2 T}{4}} = \frac{V_m}{2}$$

9.9 The voltage applied to the circuit shown in Fig. 9.5 at $t = 0$ is $100 \cos(400t + 60^\circ)$ V. The circuit resistance is 40Ω and the initial current in the 75 mH inductor is zero.

- Find $i(t)$ for $t \geq 0$.
- Write the expressions for the transient and steady-state components of $i(t)$.
- Find the numerical value of i after the switch has been closed for 1.875 ms .
- What are the maximum amplitude, frequency (in radians per second), and phase angle of the steady-state current?
- By how many degrees are the voltage and the steady-state current out of phase?

Solution

[a] The numerical values of the terms in Eq. 9.8 are

$$V_m = 100, \quad R/L = 533.33, \quad \omega L = 30$$

$$\sqrt{R^2 + \omega^2 L^2} = 50$$

$$\phi = 60^\circ, \quad \theta = \tan^{-1} 30/40, \quad \theta = 36.87^\circ$$

$$i = \left[-1.84e^{-533.33t} + 2 \cos(400t + 23.13^\circ) \right] \text{ A}, \quad t \geq 0$$

[b] Transient component $= -1.84e^{-533.33t} \text{ A}$

Steady-state component $= 2 \cos(400t + 23.13^\circ) \text{ A}$

[c] By direct substitution into Eq 9.9, $i(1.875 \text{ ms}) = 133.61 \text{ mA}$

[d] 2 A , 400 rad/s , 23.13°

[e] The current lags the voltage by 36.87° .

- 9.10 a) Verify that Eq. 9.9 is the solution of Eq. 9.8. This can be done by substituting Eq. 9.9 into the left-hand side of Eq. 9.8 and then noting that it equals the right-hand side for all values of $t > 0$. At $t = 0$, Eq. 9.9 should reduce to the initial value of the current.
- b) Because the transient component vanishes as time elapses and because our solution must satisfy the differential equation for all values of t , the steady-state component, by itself, must also satisfy the differential equation. Verify this observation by showing that the steady-state component of Eq. 9.9 satisfies Eq. 9.8.

Solution

Note:

$$L \frac{di}{dt} + Ri = V_m \cos(\omega t + \phi), \quad (9.8)$$

$$i = \frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\phi - \theta) e^{-(R/L)t} + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta), \quad (9.9)$$

[a] From Eq. 9.9 we have

$$L \frac{di}{dt} = \frac{V_m R \cos(\phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} e^{-(R/L)t} - \frac{\omega L V_m \sin(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}}$$

$$Ri = \frac{-V_m R \cos(\phi - \theta) e^{-(R/L)t}}{\sqrt{R^2 + \omega^2 L^2}} + \frac{V_m R \cos(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}}$$

$$L \frac{di}{dt} + Ri = V_m \left[\frac{R \cos(\omega t + \phi - \theta) - \omega L \sin(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} \right]$$

But

$$\frac{R}{\sqrt{R^2 + \omega^2 L^2}} = \cos \theta \quad \text{and} \quad \frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}} = \sin \theta$$

Therefore the right-hand side reduces to

$$V_m \cos(\omega t + \phi)$$

At $t = 0$, Eq. 9.9 reduces to

$$i(0) = \frac{-V_m \cos(\phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} + \frac{V_m \cos(\phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} = 0$$

$$[\mathbf{b}] \quad i_{ss} = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$

Therefore

$$L \frac{di_{ss}}{dt} = \frac{-\omega L V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin(\omega t + \phi - \theta)$$

and

$$R i_{ss} = \frac{V_m R}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$

$$\begin{aligned} L \frac{di_{ss}}{dt} + R i_{ss} &= V_m \left[\frac{R \cos(\omega t + \phi - \theta) - \omega L \sin(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} \right] \\ &= V_m \cos(\omega t + \phi) \end{aligned}$$

9.11 Use the concept of the phasor to combine the following sinusoidal functions into a single trigonometric expression:

a) $y = 100 \cos(300t + 45^\circ) + 500 \cos(300t - 60^\circ)$,

b) $y = 250 \cos(377t + 30^\circ) - 150 \sin(377t + 140^\circ)$,

c) $y = 60 \cos(100t + 60^\circ) - 120 \sin(100t - 125^\circ)$
 $+ 100 \cos(100t + 90^\circ)$, and

d) $y = 100 \cos(\omega t + 40^\circ) + 100 \cos(\omega t + 160^\circ)$
 $+ 100 \cos(\omega t - 80^\circ)$.

solution

[a] $\mathbf{Y} = 100/\underline{45^\circ} + 500/\underline{-60^\circ} = 483.86/\underline{-48.48^\circ}$

$$y = 483.86 \cos(300t - 48.48^\circ)$$

[b] $\mathbf{Y} = 250/\underline{30^\circ} - 150/\underline{50^\circ} = 120.51/\underline{4.8^\circ}$

$$y = 120.51 \cos(377t + 4.8^\circ)$$

[c] $\mathbf{Y} = 60/\underline{60^\circ} - 120/\underline{-215^\circ} + 100/\underline{90^\circ} = 152.88/\underline{32.94^\circ}$

$$y = 152.88 \cos(100t + 32.94^\circ)$$

[d] $\mathbf{Y} = 100/\underline{40^\circ} + 100/\underline{160^\circ} + 100/\underline{-80^\circ} = 0$

$$y = 0$$

9.12 A 50 Hz sinusoidal voltage with a maximum amplitude of 340 V at $t = 0$ is applied across the terminals of an inductor. The maximum amplitude of the steady-state current in the inductor is 8.5 A.

- a) What is the frequency of the inductor current?
- b) If the phase angle of the voltage is zero, what is the phase angle of the current?
- c) What is the inductive reactance of the inductor?
- d) What is the inductance of the inductor in millihenrys?
- e) What is the impedance of the inductor?

Solution

[a] 50Hz

[b] $\theta_v = 0^\circ$

$$\mathbf{I} = \frac{340/0^\circ}{j\omega L} = \frac{340}{\omega L} \angle -90^\circ = 8.5 \angle -90^\circ; \quad \theta_i = -90^\circ$$

[c] $\frac{340}{\omega L} = 8.5; \quad \omega L = 40 \Omega$

[d] $L = \frac{40}{100\pi} = \frac{400}{\pi} \text{ mH} = 127.32 \text{ mH}$

[e] $Z_L = j\omega L = j40 \Omega$

9.13 A 40 kHz sinusoidal voltage has zero phase angle and a maximum amplitude of 2.5 mV. When this voltage is applied across the terminals of a capacitor, the resulting steady-state current has a maximum amplitude of $125.67 \mu\text{A}$.

- a) What is the frequency of the current in radians per second?
- b) What is the phase angle of the current?
- c) What is the capacitive reactance of the capacitor?
- d) What is the capacitance of the capacitor in microfarads?
- e) What is the impedance of the capacitor?

Solution

$$[\text{a}] \quad \omega = 2\pi f = 80\pi \times 10^3 = 251.33 \text{ krad/s} = 251,327.41 \text{ rad/s}$$

$$[\text{b}] \quad \mathbf{I} = \frac{2.5 \times 10^{-3} \angle 0^\circ}{1/j\omega C} = j\omega C(2.5 \times 10^{-3}) \angle 0^\circ = 2.5 \times 10^{-3} \omega C \angle 90^\circ$$

$$\therefore \theta_i = 90^\circ$$

$$[\text{c}] \quad 125.66 \times 10^{-6} = 2.5 \times 10^{-3} \omega C$$

$$\frac{1}{\omega C} = \frac{2.5 \times 10^{-3}}{125.66 \times 10^{-6}} = 19.89 \Omega, \quad \therefore X_C = -19.89 \Omega$$

$$[\text{d}] \quad C = \frac{1}{19.89(\omega)} = \frac{1}{(19.89)(80\pi \times 10^3)}$$

$$C = 0.2 \times 10^{-6} = 0.2 \mu\text{F}$$

$$[\text{e}] \quad Z_c = j \left(\frac{-1}{\omega C} \right) = -j19.89 \Omega$$


9.14 The expressions for the steady-state voltage and current at the terminals of the circuit seen in Fig. P9.14 are

$$v_g = 150 \cos(8000\pi t + 20^\circ) \text{ V},$$

$$i_g = 30 \sin(8000\pi t + 38^\circ) \text{ A}$$

- What is the impedance seen by the source?
- By how many microseconds is the current out of phase with the voltage?

Figure P9.14

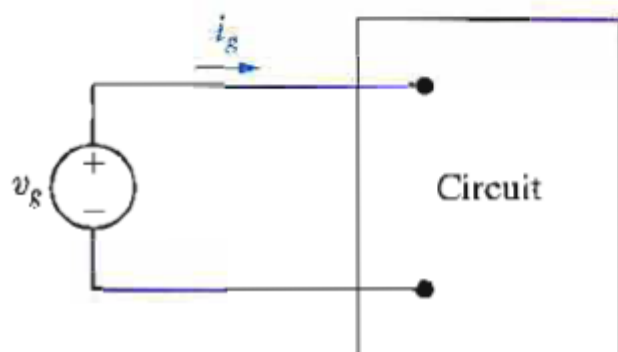

Solution

$$[a] \quad \mathbf{V}_g = 150 \angle 20^\circ; \quad \mathbf{I}_g = 30 \angle -52^\circ$$

$$\therefore Z = \frac{\mathbf{V}_g}{\mathbf{I}_g} = 5 \angle 72^\circ \Omega$$

$$[b] \quad i_g \text{ lags } v_g \text{ by } 72^\circ:$$

$$2\pi f = 8000\pi; \quad f = 4000 \text{ Hz}; \quad T = 1/f = 250 \mu\text{s}$$

$$\therefore i_g \text{ lags } v_g \text{ by } \frac{72}{360}(250) = 50 \mu\text{s}$$

9.15 A $20\ \Omega$ resistor and a $1\ \mu\text{F}$ capacitor are connected in parallel. This parallel combination is also in parallel with the series combination of a $1\ \Omega$ resistor and a $40\ \mu\text{H}$ inductor. These three parallel branches are driven by a sinusoidal current source whose current is $20 \cos(50,000t - 20^\circ)\ \text{A}$.


PSPICE

- Draw the frequency-domain equivalent circuit.
- Reference the voltage across the current source as a rise in the direction of the source current, and find the phasor voltage.
- Find the steady-state expression for $v(t)$.

Solution

$$[\text{a}] \quad j\omega L = j(5 \times 10^4)(40 \times 10^{-6}) = j2\ \Omega$$
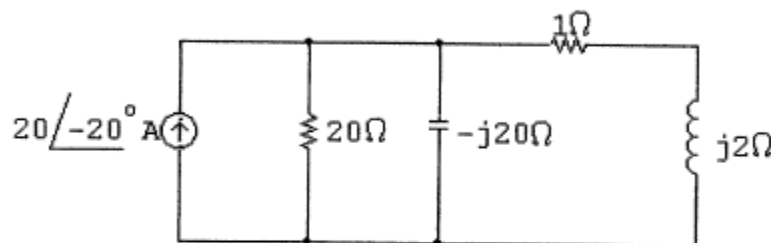
$$\frac{1}{j\omega C} = -j \frac{10^6}{5 \times 10^4} = -j20\ \Omega; \quad \mathbf{I}_g = 20 \angle -20^\circ\ \text{A}$$



$$[\text{b}] \quad \mathbf{V}_o = 20 \angle -20^\circ Z_e$$

$$Z_e = \frac{1}{Y_e}; \quad Y_e = \frac{1}{20} + j \frac{1}{20} + \frac{1}{1 + j2}$$

$$Y_e = 0.05 + j0.05 + 0.20 - j0.40 = 0.25 - j0.35\ \text{S}$$

$$Z_e = \frac{1}{0.25 - j0.35} = 2.32 \angle 54.46^\circ\ \Omega$$

$$\mathbf{V}_o = (20 \angle -20^\circ)(2.32 \angle 54.46^\circ) = 46.4 \angle 34.46^\circ\ \text{V}$$

$$[\text{c}] \quad v_o = 46.4 \cos(5 \times 10^4 t + 34.46^\circ)\ \text{V}$$


9.16 A $400\ \Omega$ resistor, a $87.5\ \text{mH}$ inductor, and a $312.5\ \text{nF}$ capacitor are connected in series. The series-connected elements are energized by a sinusoidal voltage source whose voltage is $500 \cos(8000t + 60^\circ)\ \text{V}$.

PSPICE

- Draw the frequency-domain equivalent circuit.
- Reference the current in the direction of the voltage rise across the source, and find the phasor current.
- Find the steady-state expression for $i(t)$.

Solution

[a]

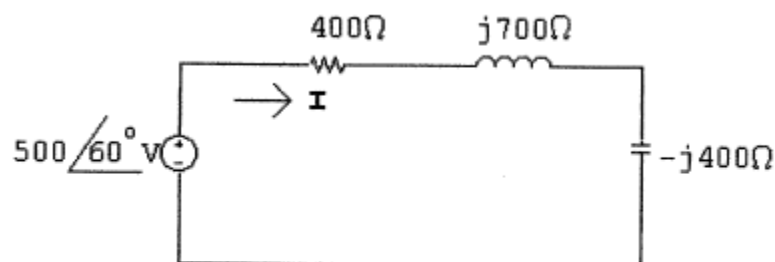

[b] $\mathbf{I} = \frac{500 \angle 60^\circ}{400 + j700 - j400} = 1 \angle 23.13^\circ \text{ A}$

[c] $i = 1 \cos(8000t + 23.13^\circ) \text{ A}$


9.17 a) Show that at a given frequency ω , the circuits in Fig. P9.17(a) and (b) will have the same impedance between the terminals a,b if

$$R_1 = \frac{R_2}{1 + \omega^2 R_2^2 C_2^2},$$

$$C_1 = \frac{1 + \omega^2 R_2^2 C_2^2}{\omega^2 R_2^2 C_2}.$$

b) Find the values of resistance and capacitance that when connected in series will have the same impedance at 80 krad/s as that of a 500 Ω resistor connected in parallel with a 25 nF capacitor.

Figure P9.17

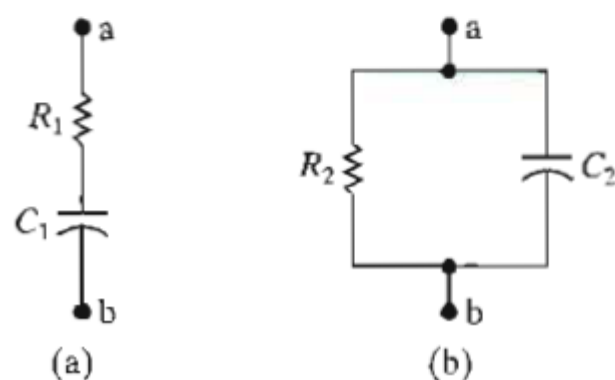

Solution

$$[a] \quad Z_1 = R_1 - j \frac{1}{\omega C_1}$$

$$Z_2 = \frac{R_2 / j\omega C_2}{R_2 + (1/j\omega C_2)} = \frac{R_2}{1 + j\omega R_2 C_2} = \frac{R_2 - j\omega R_2^2 C_2}{1 + \omega^2 R_2^2 C_2^2}$$

$$Z_1 = Z_2 \quad \text{when} \quad R_1 = \frac{R_2}{1 + \omega^2 R_2^2 C_2^2} \quad \text{and}$$

$$\frac{1}{\omega C_1} = \frac{\omega R_2^2 C_2}{1 + \omega^2 R_2^2 C_2^2} \quad \text{or} \quad C_1 = \frac{1 + \omega^2 R_2^2 C_2^2}{\omega^2 R_2^2 C_2}$$

$$[b] \quad R_1 = \frac{500}{1 + (64 \times 10^8)(25 \times 10^4)(625 \times 10^{-18})} = 250 \, \Omega$$

$$C_1 = \frac{2}{(64 \times 10^8)(25 \times 10^4)(25 \times 10^{-9})} = 50 \, \text{nF}$$

- 9.20 a) Show that at a given frequency ω , the circuits in Fig. P9.19(a) and (b) will have the same impedance between the terminals a,b if

$$R_2 = \frac{R_1^2 + \omega^2 L_1^2}{R_1}, \quad L_2 = \frac{R_1^2 + \omega^2 L_1^2}{\omega^2 L_1}.$$

(Hint: The two circuits will have the same impedance if they have the same admittance.)

- b) Find the values of resistance and inductance that when connected in parallel will have the same impedance at 10 krad/s as a 5 k Ω resistor connected in series with a 500 mH inductor.

Solution

$$[a] \quad Y_2 = \frac{1}{R_2} - \frac{j}{\omega L_2}$$

$$Y_1 = \frac{1}{R_1 + j\omega L_1} = \frac{R_1 - j\omega L_1}{R_1^2 + \omega^2 L_1^2}$$

Therefore $Y_2 = Y_1$ when

$$R_2 = \frac{R_1^2 + \omega^2 L_1^2}{R_1} \quad \text{and} \quad L_2 = \frac{R_1^2 + \omega^2 L_1^2}{\omega^2 L_1}$$


$$[b] \quad R_2 = \frac{25 \times 10^6 + 10^8(0.25)}{5 \times 10^3} = 10 \times 10^3$$

$$\therefore R_2 = 10 \text{ k}\Omega$$

$$L_2 = \frac{50 \times 10^6}{10^8(0.5)} = 1 \text{ H}$$

9.23 Find the impedance Z_{ab} in the circuit seen in Fig. P9.23. Express Z_{ab} in both polar and rectangular form.

Figure P9.23

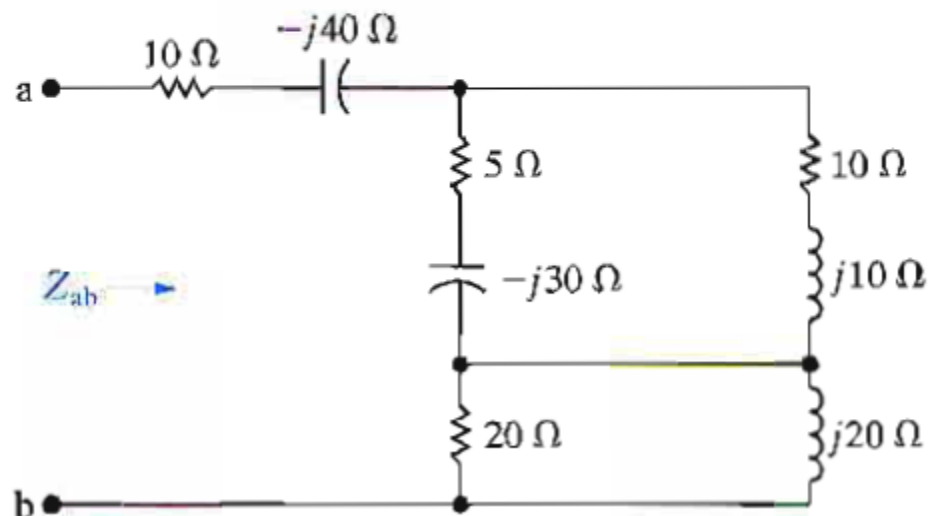

Solution

$$Z_1 = 10 - j40 \Omega$$


$$Z_2 = \frac{(5 - j10)(10 + j30)}{15 + j20} = 10 - j10 \Omega$$

$$Z_3 = \frac{20(j20)}{20 + j20} = 10 + j10 \Omega$$

$$\therefore Z_{ab} = Z_1 + Z_2 + Z_3 = 30 - j40 \Omega = 50 \angle -53.13^\circ \Omega$$

9.24 Find the admittance Y_{ab} in the circuit seen in Fig. P9.24. Express Y_{ab} in both polar and rectangular form. Give the value of Y_{ab} in millisiemens.

Figure P9.24

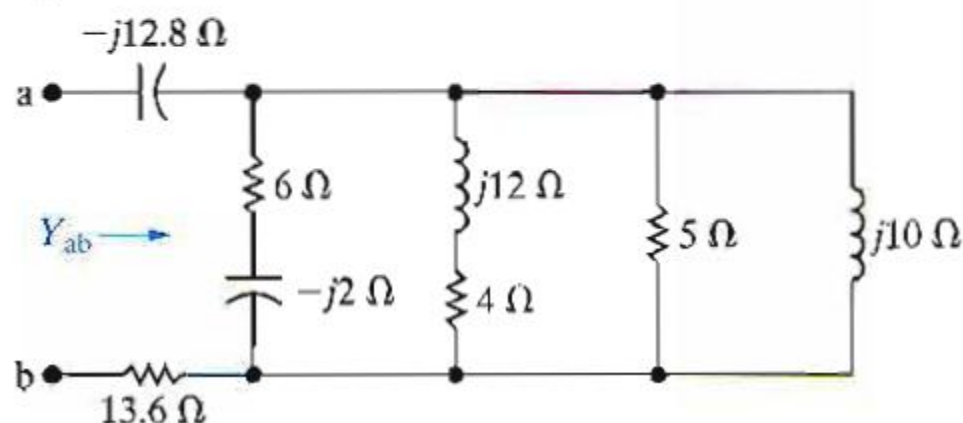

Solution

First find the admittance of the parallel branches

$$Y_p = \frac{1}{6 - j2} + \frac{1}{4 + j12} + \frac{1}{5} + \frac{1}{j10} = 0.375 - j0.125 \text{ S}$$

$$Z_p = \frac{1}{Y_p} = \frac{1}{0.375 - j0.125} = 2.4 + j0.8 \Omega$$

$$Z_{ab} = -j12.8 + 2.4 + j0.8 + 13.6 = 16 - j12 \Omega$$


$$Y_{ab} = \frac{1}{Z_{ab}} = \frac{1}{16 - j12} = 0.04 + j0.03 \text{ S}$$

$$= 40 + j30 \text{ mS} = 50/\underline{36.87^\circ} \text{ mS}$$

- 9.25** Find the steady-state expression for $i_o(t)$ in the circuit in Fig. P9.25 if $v_s = 750 \cos 5000t$ mV.

PSPICE

Figure P9.25

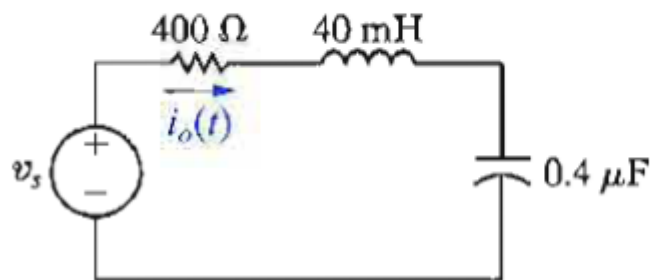

Solution

$$Z = 400 + j(5)(40) - j \frac{1000}{(5)(0.4)} = 500 \angle -36.87^\circ \Omega$$

$$I_o = \frac{750 \angle 0^\circ \times 10^{-3}}{500 \angle -36.87^\circ} = 1.5 \angle 36.87^\circ \text{ mA}$$


$$i_o(t) = 1.5 \cos(5000t + 36.87^\circ) \text{ mA}$$

- 9.26** The circuit shown in Fig. P9.26 is operating in the sinusoidal steady state. Find the value of ω if

$$i_o = 100 \sin(\omega t + 81.87^\circ) \text{ mA},$$

$$v_g = 50 \cos(\omega t - 45^\circ) \text{ V}.$$

Figure P9.26

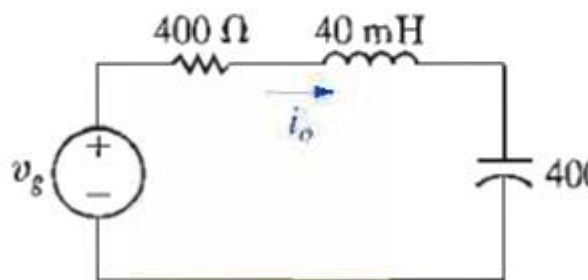

Solution

$$V_g = 50 \angle -45^\circ \text{ V}; \quad I_g = 100 \angle -8.13^\circ \text{ mA}$$

$$Z = \frac{V_g}{I_g} = 500 \angle -36.87^\circ \Omega = 400 - j300 \Omega$$

$$Z = 400 + j \left(0.04\omega - \frac{2.5 \times 10^6}{\omega} \right)$$

$$\therefore 0.04\omega - \frac{2.5 \times 10^6}{\omega} = -300$$


$$\therefore \omega^2 + 7500\omega - 62.5 \times 10^6 = 0$$

$$\therefore \omega = -3750 \pm \sqrt{(3750)^2 + 62.5 \times 10^6} = -3750 \pm 8750$$

$$\omega > 0, \quad \therefore \omega = 5000 \text{ rad/s}$$

Find the steady-state expression for v_o in the circuit of Fig. P9.27 if $i_g = 200 \cos 5000t$ mA.

Figure P9.27

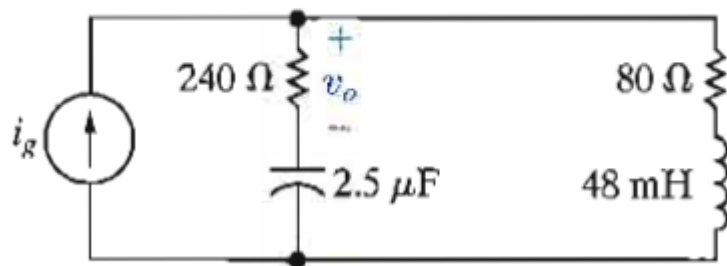


Solution

$$Z_L = j(5000)(48 \times 10^{-3}) = j240 \Omega$$

$$Z_C = \frac{-j}{(5000)(2.5 \times 10^{-6})} = -j80 \Omega$$

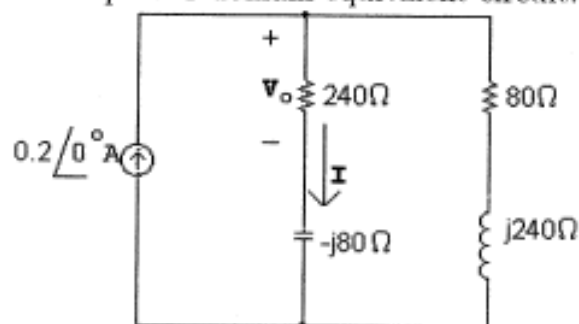Construct the phasor domain equivalent circuit:



Using current division:

$$\mathbf{I} = \frac{(80 + j240)}{240 - j80 + 80 + j240}(0.2) = 0.1 + j0.1 \text{ A}$$


$$\mathbf{V}_o = 240\mathbf{I} = 24 + j24 = 33.94 \angle 45^\circ$$

$$v_o = 33.94 \cos(5000t + 45^\circ) \text{ V}$$

9.28 The circuit in Fig. P9.28 is operating in the sinusoidal steady state. Find the steady-state expression for $v_o(t)$ if $v_g = 64 \cos 8000t$ V.

PSICE

Figure P9.28

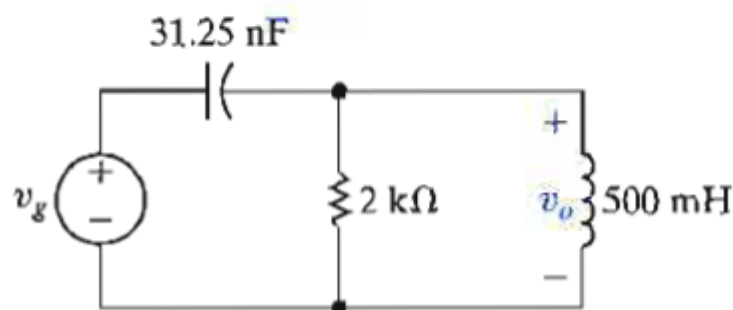


Solution

$$\frac{1}{j\omega C} = \frac{10^9}{(31.25)(8000)} = -j4000 \Omega$$

$$j\omega L = j8000(500)10^{-3} = j4000 \Omega$$
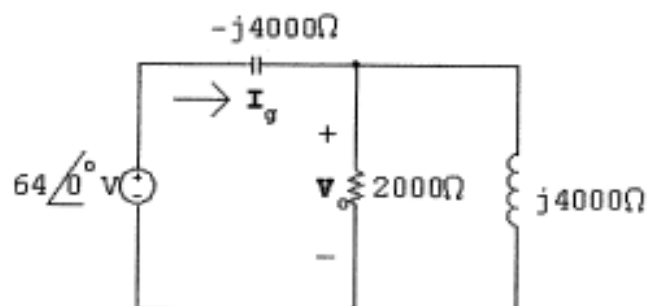
$$\mathbf{V}_g = 64\angle 0^\circ \text{ V}$$



$$Z_e = \frac{(2000)(j4000)}{2000 + j4000} = 1600 + j800 \Omega$$

$$Z_T = 1600 + j800 - j4000 = 1600 - j3200 \Omega$$

$$\mathbf{I}_g = \frac{64\angle 0^\circ}{1600 - j3200} = 8 + j16 \text{ mA}$$

$$\mathbf{V}_o = Z_e \mathbf{I}_g = (1600 + j800)(0.008 + j0.016) = j32 = 32\angle 90^\circ \text{ V}$$


$$v_o = 32 \cos(8000t + 90^\circ) \text{ V}$$

9.29 The phasor current \mathbf{I}_a in the circuit shown in

PSPICE Fig. P9.29 is $40 \angle 0^\circ$ mA.


- Find \mathbf{I}_b , \mathbf{I}_c , and \mathbf{V}_g .
- If $\omega = 800$ rad/s, write the expressions for $i_b(t)$, $i_c(t)$, and $v_g(t)$.

Figure P9.29

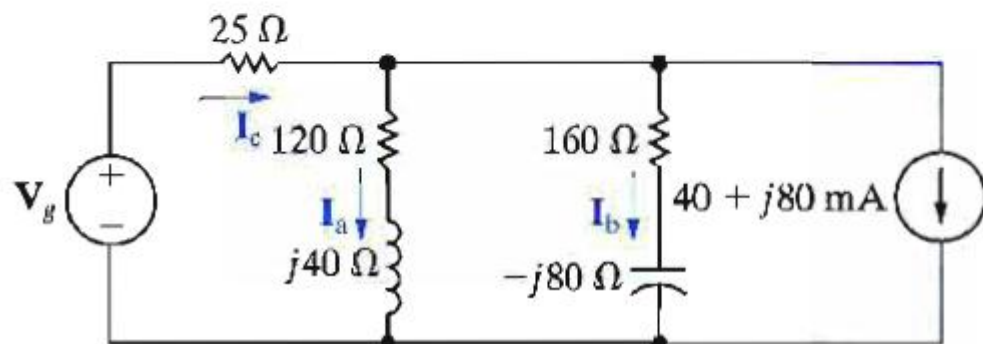

Solution

[a]

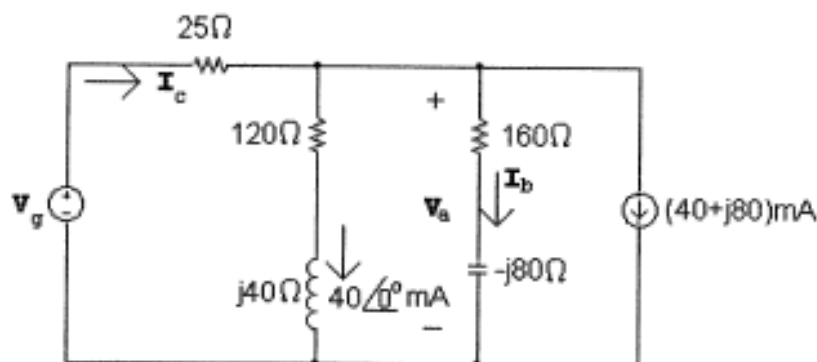

$$\mathbf{V}_a = (120 + j40)(0.04 \angle 0^\circ) = 4.8 + j1.6 \text{ V}$$

$$\mathbf{I}_b = \frac{4.8 + j1.6}{160 - j80} = 20 + j20 \text{ mA}$$

$$\mathbf{I}_c = 40 \angle 0^\circ + (20 + j20) + (40 + j80) \text{ mA} = 100 + j100 \text{ mA}$$

$$\mathbf{V}_g = 25\mathbf{I}_c + \mathbf{V}_a = 25(0.100 + j0.100) + 4.8 + j1.6 = 7.3 + j4.1 \text{ V}$$


[b] $i_b = 28.28 \cos(800t + 45^\circ) \text{ mA}$

$$i_c = 141.42 \cos(800t + 45^\circ) \text{ mA}$$

$$v_g = 8.37 \cos(800t + 29.32^\circ) \text{ V}$$

- 9.30** a) For the circuit shown in Fig. P9.30, find the steady-state expression for v_o if $i_g = 5 \cos(8 \times 10^5 t)$ A.
 b) By how many nanoseconds does v_o lag i_g ?

Figure P9.30

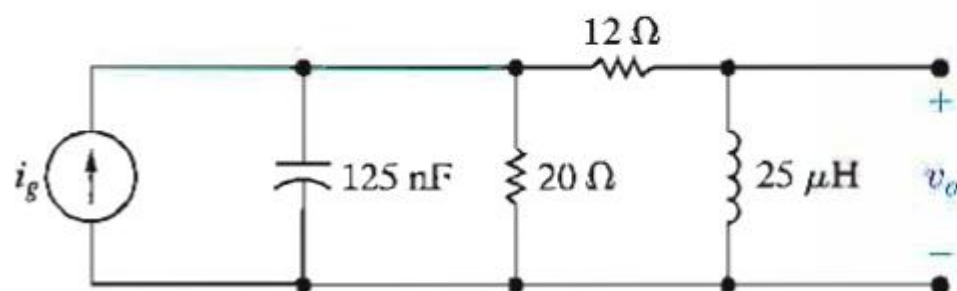

.Solution


$$[a] \frac{1}{j\omega C} = \frac{10^9}{j8 \times 10^5(125)} = -j10 \Omega$$

$$j\omega L = j8 \times 10^5(25 \times 10^{-6}) = j20 \Omega$$

$$Z_e = \frac{(-j10)(20)}{20 - j10} = 4 - j8 \Omega$$

$$\mathbf{I}_g = 5 \angle 0^\circ$$
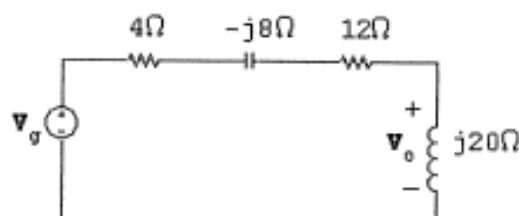
$$\mathbf{V}_g = \mathbf{I}_g Z_e = 5(4 - j8) = 20 - j40 \text{ V}$$



$$\mathbf{V}_o = \frac{(20 - j40)(j20)}{(16 + j12)} = 44 - j8 = 44.72 \angle -10.30^\circ \text{ V}$$

$$v_o = 44.72 \cos(8 \times 10^5 t - 10.30^\circ) \text{ V}$$

$$[b] \omega = 2\pi f = 8 \times 10^5; \quad f = \frac{4 \times 10^5}{\pi}$$

$$T = \frac{1}{f} = \frac{\pi}{4 \times 10^5} = 2.5\pi \mu\text{s}$$


$$\therefore \frac{10.30}{360}(2.5\pi) = 224.82 \text{ ns}$$

$$\therefore v_o \text{ lags } i_g \text{ by } 224.82 \text{ ns}$$

9.31 The circuit in Fig. P9.31 is operating in the sinusoidal steady state. Find $v_o(t)$ if $i_s(t) = 15 \cos 8000t$ mA.

PSPICE

Figure P9.31

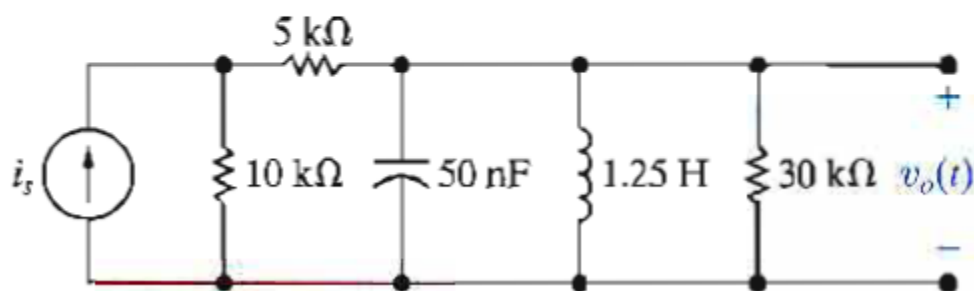


Solution

P 9.31 $\mathbf{I}_s = 15 \angle 0^\circ \text{ mA}$

$$\frac{1}{j\omega C} = \frac{10^6}{j0.05(8000)} = -j2500 \Omega$$

$$j\omega L = j8000(1.25) = j10,000 \Omega$$

After two source transformations we have

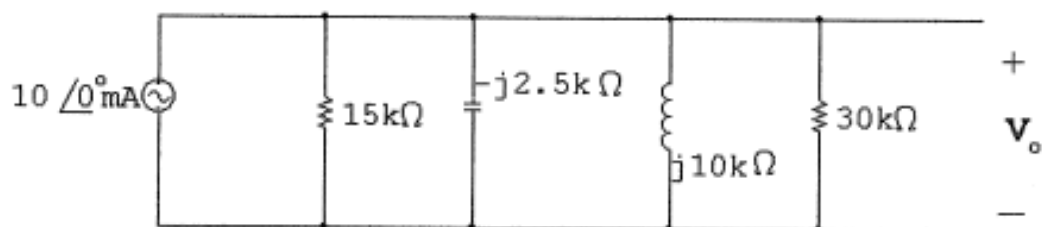

$$15 \text{ k}\Omega \parallel 30 \text{ k}\Omega = 10 \text{ k}\Omega$$

$$\mathbf{Y}_o = \frac{10^{-3}}{10} + \frac{1}{-j2500} + \frac{1}{j10^4} = 10^{-4}(1 + j3)$$


$$\mathbf{Z}_o = \frac{10^4}{1 + j3} = (1 - j3) \text{ k}\Omega$$

$$\mathbf{V}_o = \mathbf{I}_s \mathbf{Z}_o = (10)(1 - j3) = 10 - j30 = 31.62 \angle -71.57^\circ \text{ V}$$

$$v_o = 31.62 \cos(8000t - 71.57^\circ) \text{ V}$$

9.34 Find Z_{ab} for the circuit shown in Fig P9.34.


Figure P9.34

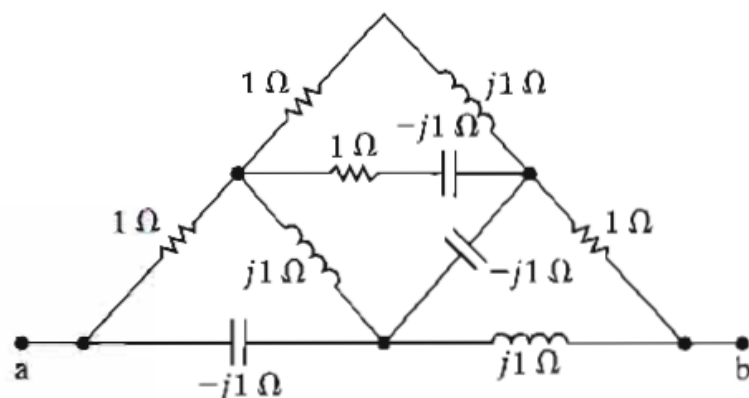

Simplify the top triangle using series and parallel combinations:

$$(1 + j1) \parallel (1 - j1) = 1 \Omega$$

Convert the lower left delta to a wye:

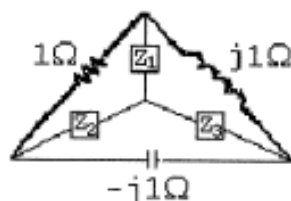

$$Z_1 = \frac{(j1)(1)}{1 + j1 - j1} = j1 \Omega$$

$$Z_2 = \frac{(-j1)(1)}{1 + j1 - j1} = -j1 \Omega$$

$$Z_3 = \frac{(j1)(-j1)}{1 + j1 - j1} = 1 \Omega$$

Convert the lower right delta to a wye:




$$Z_4 = \frac{(-j1)(1)}{1 + j1 - j1} = -j1 \Omega$$

$$Z_5 = \frac{(-j1)(j1)}{1 + j1 - j1} = 1 \Omega$$

$$Z_6 = \frac{(j1)(1)}{1 + j1 - j1} = j1 \Omega$$

The resulting circuit is shown below:

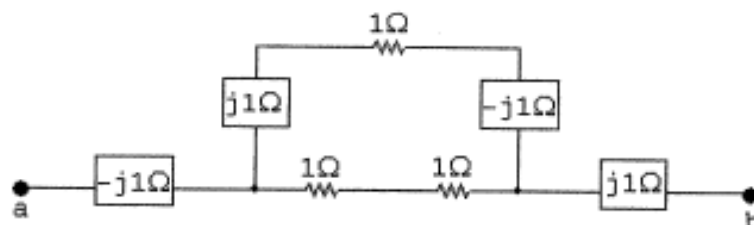

Simplify the middle portion of the circuit by making series and parallel combinations:

$$(1 + j1 - j1) \parallel (1 + 1) = 1 \parallel 2 = 2/3 \Omega$$


$$Z_{ab} = -j1 + 2/3 + j1 = 2/3 \Omega$$

9.35 The frequency of the sinusoidal voltage source in the circuit in Fig. P9.35 is adjusted until the current i_o is in phase with v_g .

PSICE

- Find the frequency in hertz.
- Find the steady-state expression for i_o (at the frequency found in [a]) if $v_g = 10 \cos \omega t$ V.

Figure P9.35

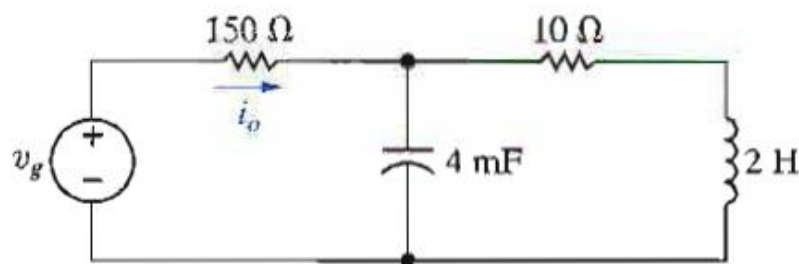

$$\begin{aligned}
 \text{[a]} \quad Y_p &= \frac{1}{10 + j2\omega} + j4 \times 10^{-3}\omega \\
 &= \frac{10 - j2\omega}{100 + 4\omega^2} + j4 \times 10^{-3}\omega \\
 &= \frac{10}{100 + 4\omega^2} - \frac{j2\omega}{100 + 4\omega^2} + j4 \times 10^{-3}\omega
 \end{aligned}$$

Y_p is real when

$$4 \times 10^{-3}\omega = \frac{2\omega}{100 + 4\omega^2}$$

$$\text{or} \quad \omega^2 = 100; \quad \omega = 10 \text{ rad/s}; \quad f = 5/\pi = 1.59 \text{ Hz}$$

$$\text{[b]} \quad Y_p(10 \text{ rad/s}) = \frac{10}{500} = 20 \text{ mS}$$

$$Z_p(10 \text{ rad/s}) = \frac{10^3}{20} = 50 \Omega$$

$$Z(10 \text{ rad/s}) = 50 + 150 = 200 \Omega$$

$$I_o = \frac{V_g}{200} \text{ A} = \frac{10 \angle 0^\circ}{200} = 50 \angle 0^\circ \text{ mA}$$


$$i_o = 50 \cos 10t \text{ mA}$$

9.37 The frequency of the sinusoidal current source in the circuit in Fig. P9.37 is adjusted until v_o is in phase with i_g .

PSICE

- What is the value of ω in radians per second?
- If $i_g = 2.5 \cos \omega t$ mA (where ω is the frequency found in [a]), what is the steady-state expression for v_o ?

Figure P9.37

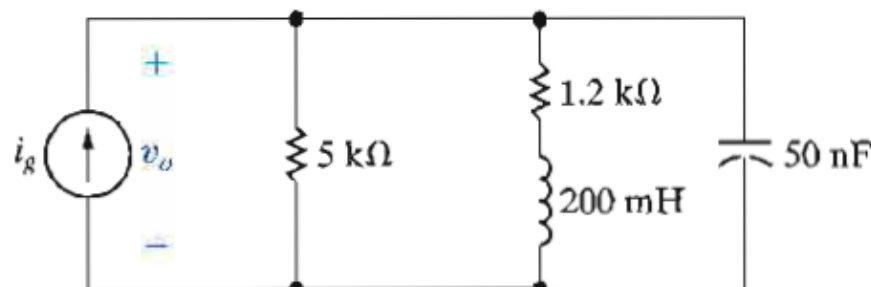

$$[a] \quad Y_1 = \frac{1}{5000} = 0.2 \times 10^{-3} \text{ S}$$

$$Y_2 = \frac{1}{1200 + j0.2\omega}$$

$$= \frac{1200}{1.44 \times 10^6 + 0.04\omega^2} - j \frac{0.2\omega}{1.44 \times 10^6 + 0.04\omega^2}$$

$$Y_3 = j\omega 50 \times 10^{-9}$$

$$Y_T = Y_1 + Y_2 + Y_3$$

For i_g and v_o to be in phase the j component of Y_T must be zero; thus,

$$\omega 50 \times 10^{-9} = \frac{0.2\omega}{1.44 \times 10^6 + 0.04\omega^2}$$

or

$$0.04\omega^2 + 1.44 \times 10^6 = \frac{0.2 \times 10^9}{50} = 4 \times 10^6$$

$$\therefore 0.04\omega^2 = 2.56 \times 10^6 \quad \therefore \omega = 8000 \text{ rad/s} = 8 \text{ krad/s}$$

$$[b] \quad Y_T = 0.2 \times 10^{-3} + \frac{1200}{1.44 \times 10^6 + 0.04(64) \times 10^6} = 0.5 \times 10^{-3} \text{ S}$$


$$\therefore Z_T = 2000 \Omega$$

$$\mathbf{V}_o = (2.5 \times 10^{-3} \angle 0^\circ)(2000) = 5 \angle 0^\circ$$

$$v_o = 5 \cos 8000t \text{ V}$$

- 9.39** a) The source voltage in the circuit in Fig. P9.39 is $v_g = 96 \cos 10,000t$ V. Find the values of L such that i_g is in phase with v_g when the circuit is operating in the steady state.
- b) For the values of L found in (a), find the steady-state expressions for i_g .

Figure P9.39

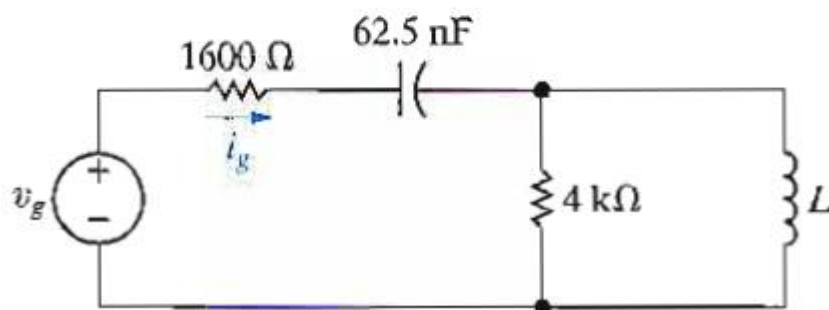

$$[a] \quad Z_1 = 1600 - j \frac{10^9}{10^4(62.5)} = 1600 - j1600 \, \Omega$$

$$Z_1 = \frac{4000(j10^4 L)}{4000 + j10^4 L} = \frac{4 \times 10^5 L^2 + j16 \times 10^4 L}{16 + 100L^2}$$

$$Z_T = Z_1 + Z_2 = 1600 + \frac{4 \times 10^5 L^2}{16 + 100L^2} - j1600 + j \frac{16 \times 10^4 L}{16 + 100L^2}$$

Z_T is resistive when

$$\frac{16 \times 10^4 L}{16 + 100L^2} = 1600 \quad \text{or}$$

$$L^2 - L + 0.16 = 0$$

Solving, $L_1 = 0.8$ H and $L_2 = 0.2$ H.

[b] When $L = 0.8$ H:

$$Z_T = 1600 + \frac{4 \times 10^5(0.64)}{16 + 64} = 4800 \, \Omega$$

$$I_g = \frac{96/0^\circ}{4.8} \times 10^{-3} = 20/0^\circ \text{ mA}$$

$$i_g = 20 \cos 10,000t \text{ mA}$$


When $L = 0.2$ H:

$$Z_T = 1600 + \frac{4 \times 10^5(0.04)}{16 + 4} = 2400 \, \Omega$$

$$i_g = 40 \cos 10,000t \text{ mA}$$

9.40 Use source transformations to find the Thévenin equivalent circuit with respect to the terminals a,b for the circuit shown in Fig. P9.40.

Figure P9.40

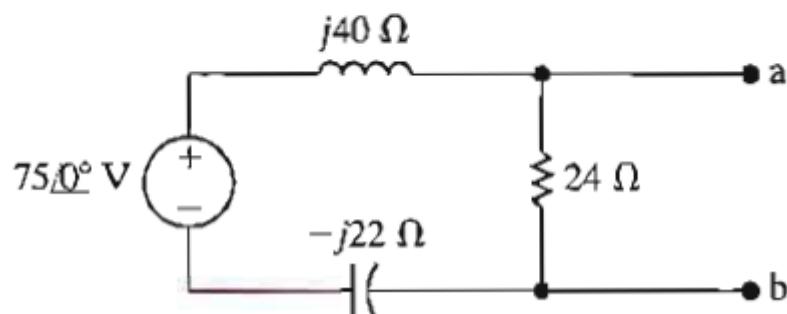

Step 1 to Step 2:





$$\frac{75\angle 0^\circ}{j18} = -j4.167 = 4.167\angle -90^\circ \text{ A}$$

Step 2 to Step 3:

$$(j18)\parallel 24 = \frac{(j18)(24)}{24 + j18} = 8.64 + j11.52 \Omega$$


Step 3 to Step 4:
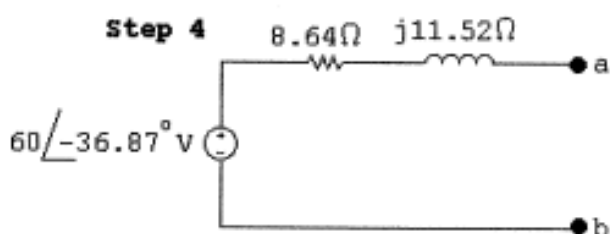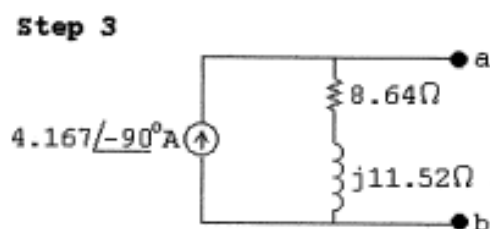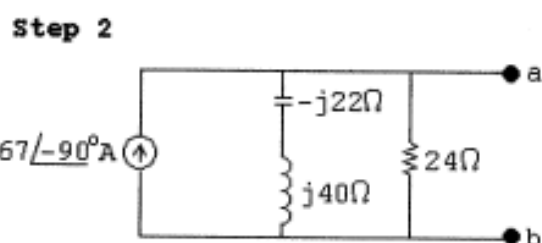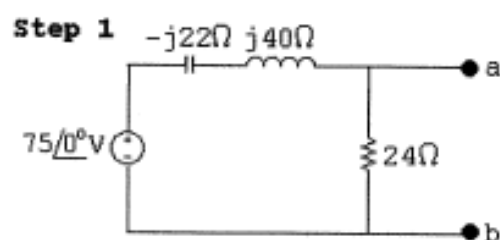
$$(4.167\angle -90^\circ)(8.64 + j11.52) = 60\angle -36.87^\circ \text{ V}$$



9.41 Use source transformations to find the Norton equivalent circuit with respect to the terminals a,b for the circuit shown in Fig. P9.41.

Figure P9.41

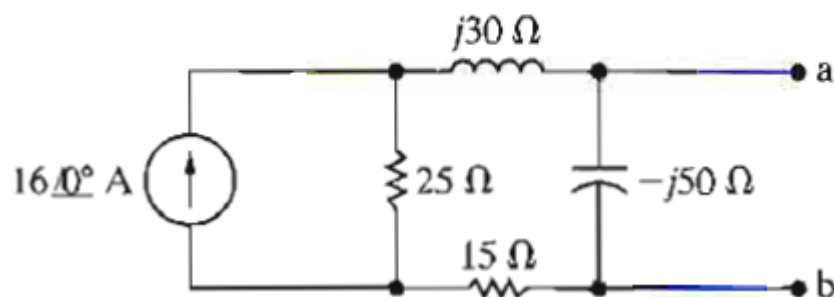

P 9.41 Step 1 to Step 2:

$$(16\angle 0^\circ)(25) = 400\angle 0^\circ \text{ V}$$

Step 2 to Step 3:

$$25 + 15 + j30 = (40 + j30) \Omega$$


Step 3 to Step 4:

$$\frac{400\angle 0^\circ}{(40 + j30)} = 8\angle -36.87^\circ \text{ A}$$


Step 4 to Step 5:

$$(40 + j30 \parallel -j50) = \frac{(-j50)(40 + j30)}{40 + j30 - j50} = 50 - j25 \Omega$$


Step 1

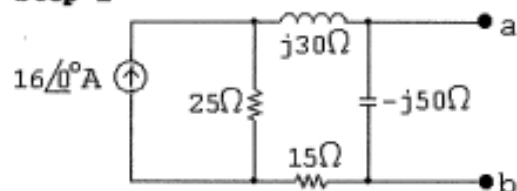


Step 2

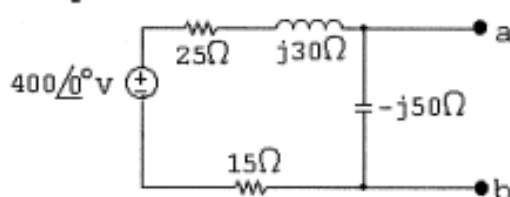


Step 3

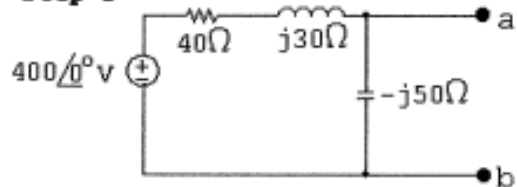

Step 4

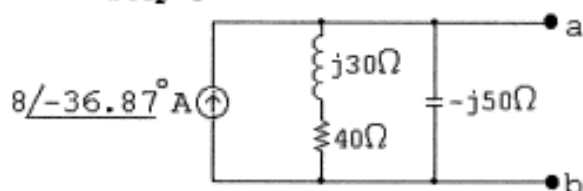


Step 5

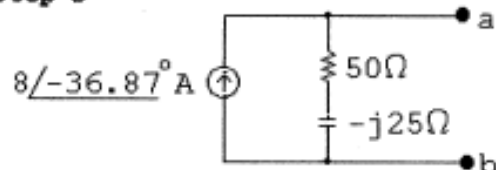

9.42 The sinusoidal voltage source in the circuit in Fig. P9.42 is developing a voltage equal to $22.36 \cos(5000t + 26.565^\circ)$ V.


- Find the Thévenin voltage with respect to the terminals a,b.
- Find the Thévenin impedance with respect to the terminals a,b.
- Draw the Thévenin equivalent.

Figure P9.42

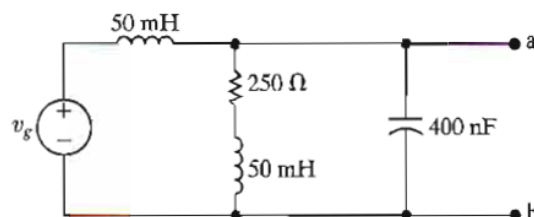

P 9.42 [a] $j\omega L = j(5000)(50) \times 10^{-3} = j250 \Omega$
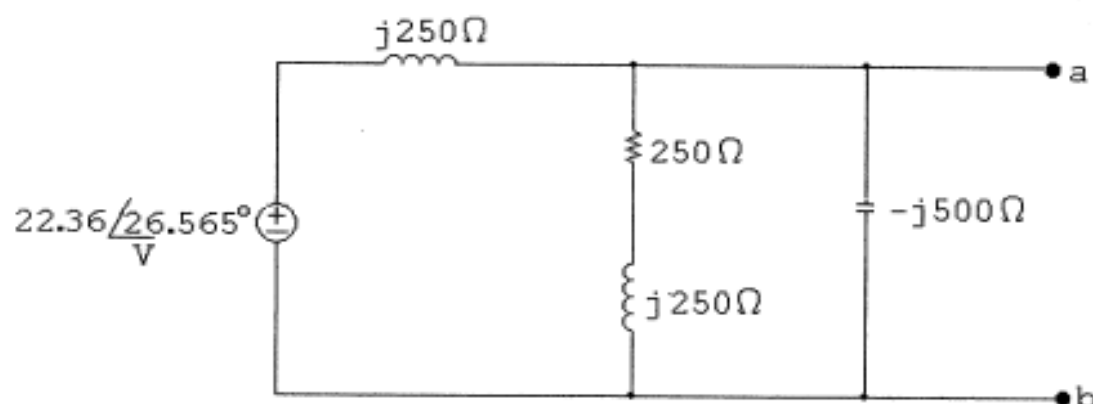
$$\frac{1}{j\omega C} = -j \frac{1}{(5000)(400 \times 10^{-9})} = -j500 \Omega$$



Using voltage division,

$$V_{ab} = \frac{(250 + j250) \parallel (-j500)}{j250 + (250 + j250) \parallel (-j500)} (22.36 \angle 26.565^\circ) = 20 \angle 0^\circ$$

$$V_{Th} = V_{ab} = 20 \angle 0^\circ \text{ V}$$


- [b] Remove the voltage source and combine impedances in parallel to find

$$Z_{Th} = Z_{ab}:$$

$$Y_{ab} = \frac{1}{j250} + \frac{1}{250 + j250} + \frac{1}{-j500} = 2 - j4 \text{ mS}$$



$$Z_{Th} = Z_{ab} = \frac{1}{Y_{ab}} = 100 + j200 \Omega$$

[c]

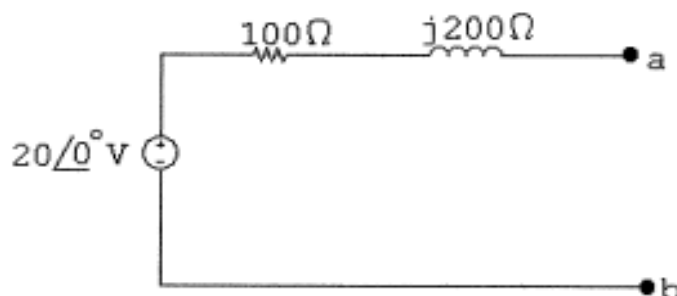

9.43 Find the Thévenin equivalent circuit with respect to the terminals a,b for the circuit shown in Fig. P9.43.

Figure P9.43

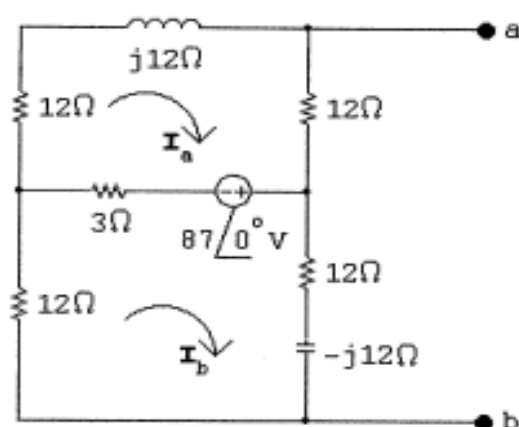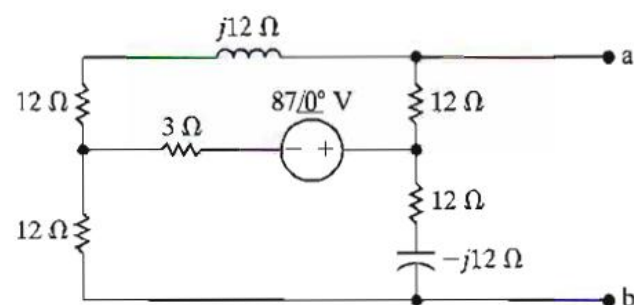

$$(27 + j12)\mathbf{I}_a - 3\mathbf{I}_b = -87\angle 0^\circ$$


$$-3\mathbf{I}_a + (27 - j12)\mathbf{I}_b = 87\angle 0^\circ$$

Solving,

$$\mathbf{I}_a = -2.4167 + j1.21; \quad \mathbf{I}_b = 2.4167 + j1.21$$

$$\mathbf{V}_{Th} = 12\mathbf{I}_a + (12 - j12)\mathbf{I}_b = 14.5\angle 0^\circ \text{ V}$$

Short Circuit Test:

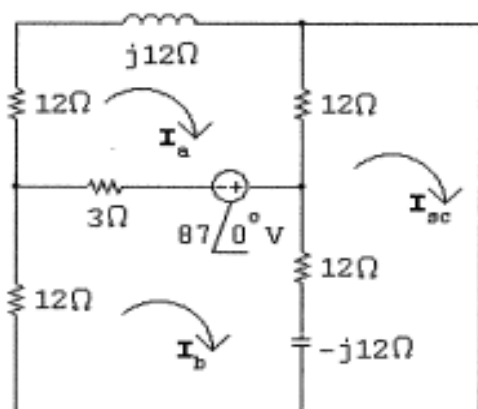

$$(27 + j12)\mathbf{I}_a - 3\mathbf{I}_b - 12\mathbf{I}_{sc} = -87$$

$$-3\mathbf{I}_a + (27 - j12)\mathbf{I}_b - (12 - j12)\mathbf{I}_{sc} = 87$$


$$-12\mathbf{I}_a - (12 - j12)\mathbf{I}_b + (24 - j12)\mathbf{I}_{sc} = 0$$

Solving,

$$\mathbf{I}_{sc} = 1\angle 0^\circ$$

$$Z_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{14.5 \angle 0^\circ}{1 \angle 0^\circ} = 14.5 \Omega$$

Alternate calculation for Z_{Th} :

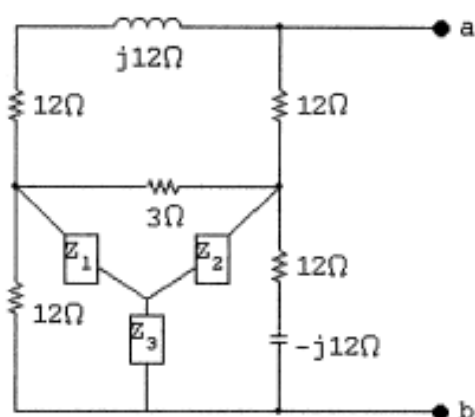


$$\sum Z = 12 + 3 + 12 - j12 = 27 - j12$$

$$Z_1 = \frac{36}{27 - j12} = \frac{12}{9 - j4}$$

$$Z_2 = \frac{36 - j36}{27 - j12} = \frac{12 - j12}{9 - j4}$$
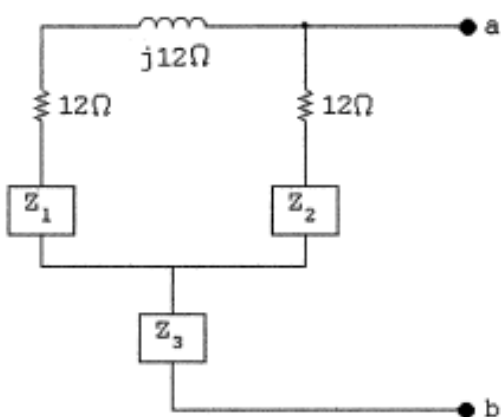
$$Z_3 = \frac{12(12 - j12)}{27 - j12} = \frac{48 - j48}{9 - j4}$$



$$Z_a = 12 + j12 + \frac{12}{9 - j4} = \frac{12(14 + j5)}{9 - j4}$$


$$Z_b = 12 + \frac{12 - j12}{9 - j4} = \frac{12(10 - j5)}{9 - j4}$$

$$Z_a \parallel Z_b = \frac{165 - j20}{18 - j8}$$


$$Z_3 + Z_a \parallel Z_b = \frac{48 - j48}{9 - j4} + \frac{165 - j20}{18 - j8} = 14.5 \Omega$$

- 9.44** The device in Fig. P9.44 is represented in the frequency domain by a Norton equivalent. When an inductor having an impedance of $j100\ \Omega$ is connected across the device, the value of \mathbf{V}_0 is $100\angle 120^\circ\text{ mV}$. When a capacitor having an impedance of $-j100\ \Omega$ is connected across the device, the value of \mathbf{I}_0 is $-3\angle 210^\circ\text{ mA}$. Find the Norton current \mathbf{I}_N and the Norton impedance \mathbf{Z}_N .


Figure P9.44

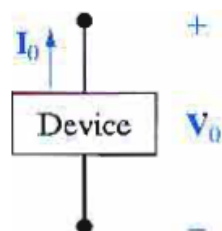

P 9.44

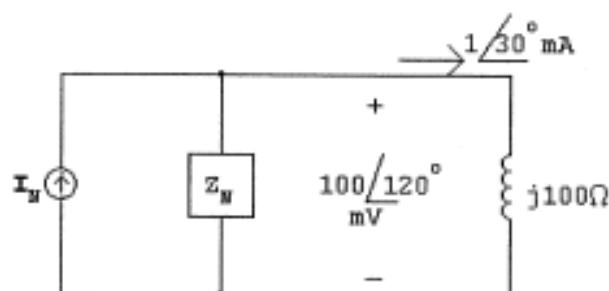
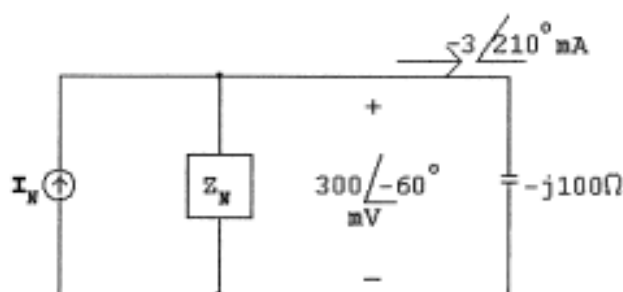
$$\mathbf{I}_N = \frac{0.1\angle 120^\circ}{\mathbf{Z}_N} + 1\angle 30^\circ\text{ mA}, \quad \mathbf{Z}_N \text{ in k}\Omega$$




$$\mathbf{I}_N = \frac{0.3\angle -60^\circ}{\mathbf{Z}_N} + (-3\angle 210^\circ)\text{ mA}, \quad \mathbf{Z}_N \text{ in k}\Omega$$

$$\frac{0.1\angle 120^\circ}{\mathbf{Z}_N} + 1\angle 30^\circ = \frac{0.3\angle -60^\circ}{\mathbf{Z}_N} + (-3\angle 210^\circ)$$

$$\frac{0.3\angle -60^\circ - 0.1\angle 120^\circ}{\mathbf{Z}_N} = 1\angle 30^\circ + 3\angle 210^\circ$$


$$\mathbf{Z}_N = \frac{0.3\angle -60^\circ - 0.1\angle 120^\circ}{1\angle 30^\circ + 3\angle 210^\circ} = 0.2\angle 90^\circ = j0.2\text{ k}\Omega$$
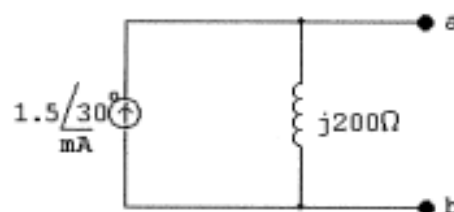
$$\mathbf{I}_N = \frac{0.1\angle 120^\circ}{0.2\angle 90^\circ} + 1\angle 30^\circ = 1.5\angle 30^\circ\text{ mA}$$




- 9.45 Find Z_{ab} in the circuit shown in Fig. P9.45 when the circuit is operating at a frequency of 1.6 Mrad/s.

Figure P9.45

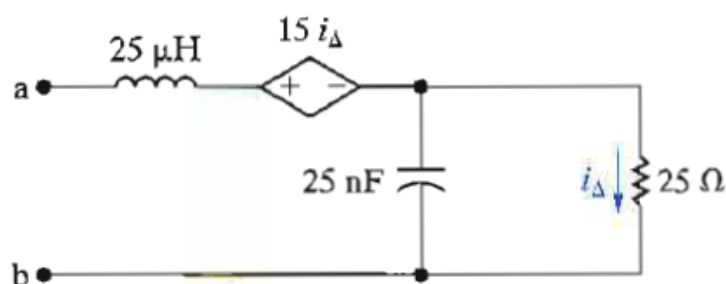

$$j\omega L = j1.6 \times 10^6 (25 \times 10^{-6}) = j40 \Omega$$
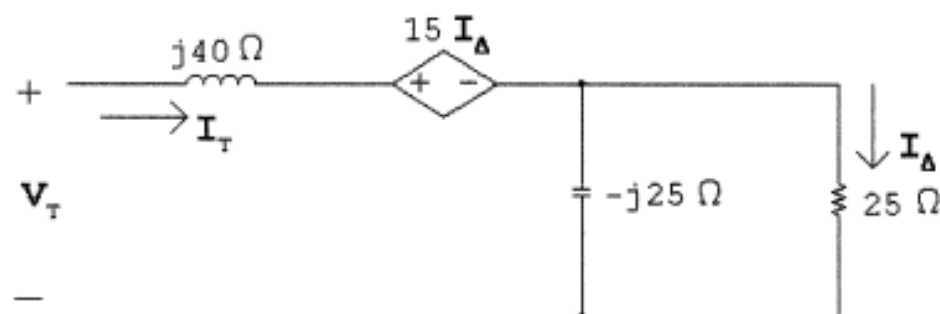
$$\frac{1}{j\omega C} = \frac{10^{-6} \times 10^9}{j1.6(25)} = -j25 \Omega$$



$$\mathbf{V}_T = j40\mathbf{I}_T + 15\mathbf{I}_\Delta + 25\mathbf{I}_\Delta$$


$$\mathbf{I}_\Delta = \frac{\mathbf{I}_T(-j25)}{25 - j25} = \frac{-j\mathbf{I}_T}{1 - j1}$$

$$\mathbf{V}_T = j40\mathbf{I}_T + 40 \frac{(-j\mathbf{I}_T)}{1 - j1}$$

$$\frac{\mathbf{V}_T}{\mathbf{I}_T} = Z_{ab} = j40 + 20(-j)(1 + j) = 20 + j20 \Omega = 28.28 \angle 45^\circ \Omega$$


- 9.46** Find the Thévenin impedance seen looking into the terminals a,b of the circuit in Fig. P9.46 if the frequency of operation is 25 krad/s.

Figure P9.46

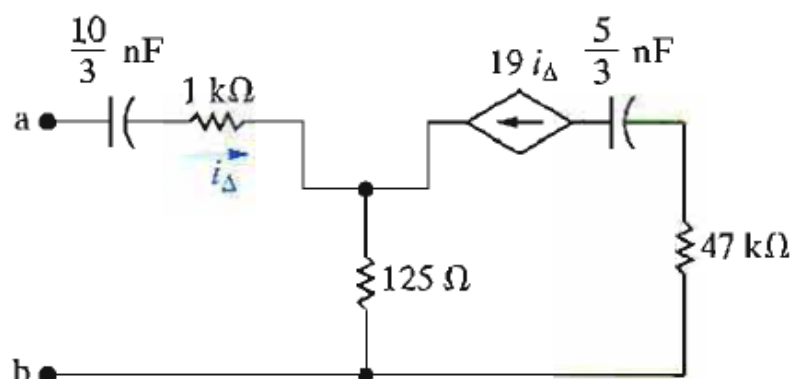

$$\frac{1}{\omega C_1} = \frac{(10^{-3})(10^9)}{25(10/3)} = 12 \text{ k}\Omega$$
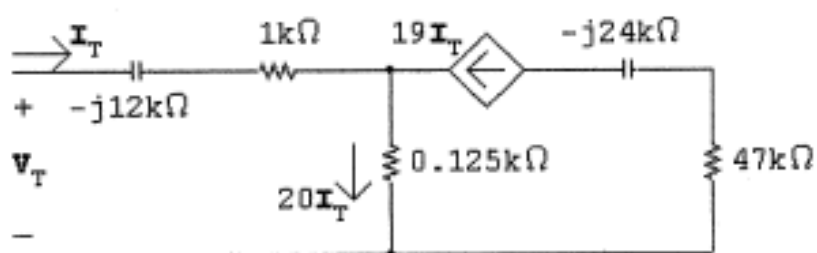
$$\frac{1}{\omega C_2} = \frac{(10^{-3})(10^9)}{25(5/3)} = 24 \text{ k}\Omega$$




$$\mathbf{V}_T = (1 - j12)\mathbf{I}_T + 20\mathbf{I}_T(0.125)$$


$$Z_{Th} = \frac{\mathbf{V}_T}{\mathbf{I}_T} = 3.5 - j12 \text{ k}\Omega$$

9.47 Find the Norton equivalent with respect to terminals a,b in the circuit of Fig. P9.47.

Figure P9.47

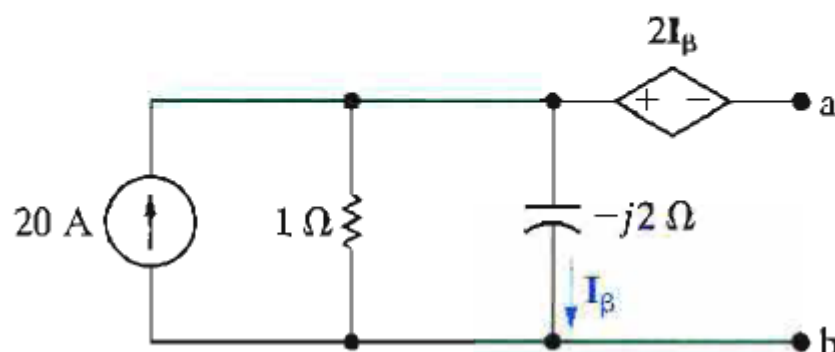

Short circuit current

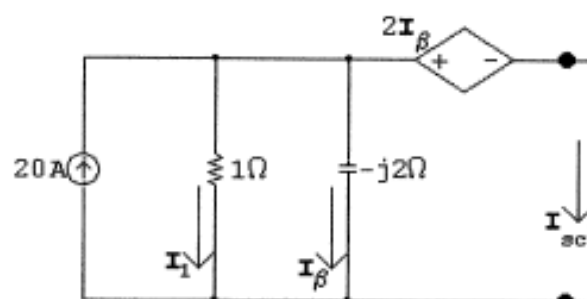


$$I_{\beta} = \frac{2I_{\beta}}{-j2}$$

$$-j2I_{\beta} = 2I_{\beta}; \quad \therefore I_{\beta} = 0$$

$$I_1 = 0; \quad \therefore I_{sc} = 20 \text{ A} = I_N$$

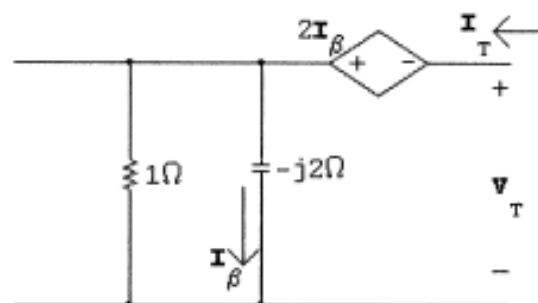The Norton impedance is the same as the Thévenin impedance. Find it using a test source





$$V_T = -2I_{\beta} - j2I_{\beta} = (-2 - j2)I_{\beta}, \quad I_{\beta} = \frac{1}{1 - j2}I_T$$

$$Z_{Th} = \frac{V_T}{I_T} = \frac{(-2 - j2)I_{\beta}}{[(1 - j2)/1]I_{\beta}} = \frac{-2 - j2}{1 - j2} = 0.4 - j1.2 \Omega$$

9.48 Find the Thévenin equivalent circuit with respect to the terminals a,b of the circuit shown in Fig. P9.48.

Figure P9.48

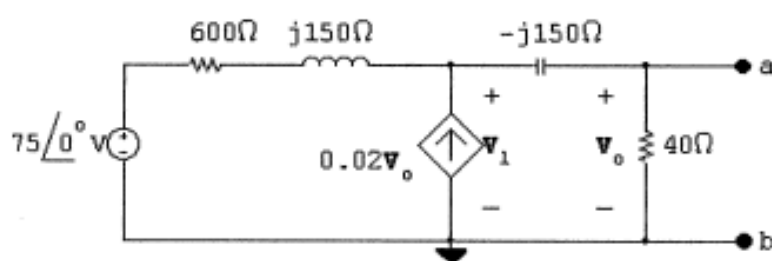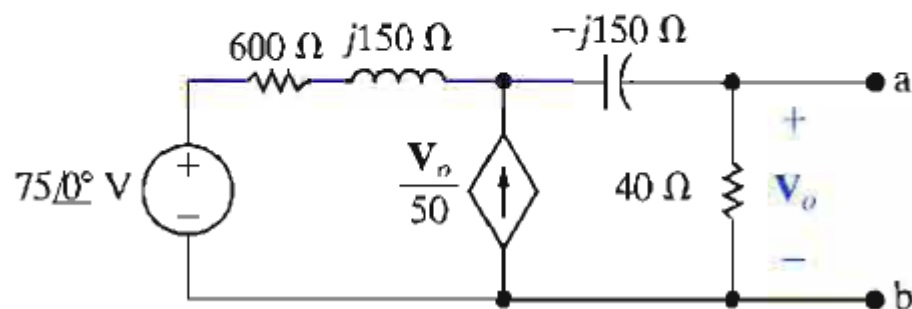

$$\frac{V_1 - 75}{150(4 + j1)} - \frac{0.02V_1(40)}{40 - j150} + \frac{V_1}{40 - j150} = 0$$


$$\therefore V_1 = \frac{75(4 - j15)}{16 - j12}$$

$$V_{Th} = \frac{40V_1}{40 - j150} = \frac{4}{4 - j15} \cdot \frac{75(4 - j15)}{16 - j12}$$

$$= \frac{75}{4 - j3} = 15\angle 36.87^\circ \text{ V}$$


$$I_{sc} = \frac{75}{600} = \frac{1}{8} \text{ A}$$
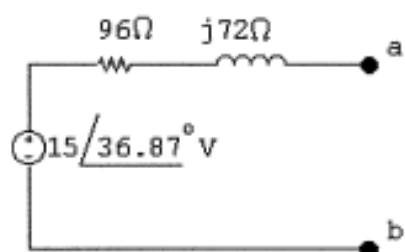
$$Z_{Th} = \frac{V_{Th}}{I_{sc}} = 120\angle 36.87^\circ = 96 + j72 \Omega$$



9.49 Find the Norton equivalent circuit with respect to the terminals a,b for the circuit shown in Fig. P9.49 when $\mathbf{V}_s = 25 \angle 0^\circ \text{ V}$.

Figure P9.49

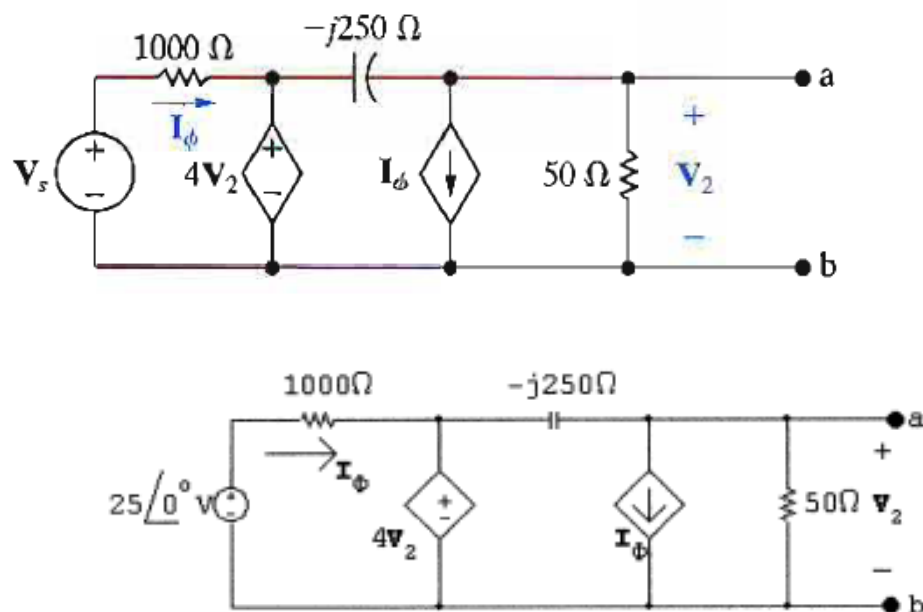

$$\frac{V_2}{50} + \frac{25 - 4V_2}{1000} + \frac{V_2 - 4V_2}{-j250} = 0$$

Solving,


$$\mathbf{V}_2 = -1 - j0.75 \text{ V} = 1.25 \angle 216.87^\circ \text{ V}$$

$$\mathbf{I}_{sc} = -\mathbf{I}_\phi = \frac{-25 \angle 0^\circ}{1000} = -25 \angle 0^\circ \text{ mA}$$

$$\mathbf{Z}_{Th} = \frac{1.25 \angle 216.87^\circ}{-25 \times 10^{-3} \angle 0^\circ} = 50 \angle 36.87^\circ \Omega = 40 + j30 \Omega$$

$$\mathbf{I}_N = \mathbf{I}_{sc} = -25 \angle 0^\circ \text{ mA}$$

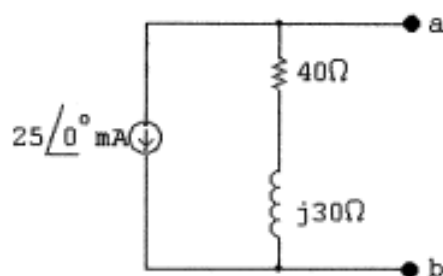
$$\mathbf{Z}_N = \mathbf{Z}_{Th} = 50 \angle 36.87^\circ = 40 + j30 \Omega$$




9.50 The circuit shown in Fig. P9.50 is operating at a frequency of 10 krad/s. Assume α is real and lies between -50 and $+50$, that is, $-50 \leq \alpha \leq 50$.

- Find the value of α so that the Thévenin impedance looking into the terminals a,b is purely resistive.
- What is the value of the Thévenin impedance for the α found in (a)?
- Can α be adjusted so that the Thévenin impedance equals $5 + j5 \Omega$? If so, what is the value of α ?
- For what values of α will the Thévenin impedance be inductive?

Figure P9.50

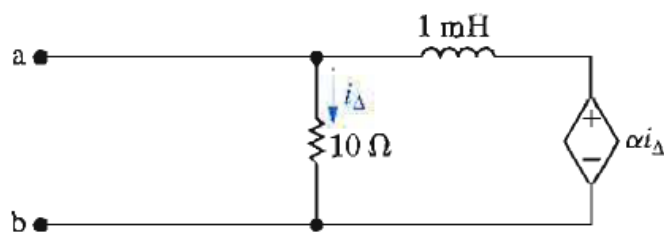

[a]

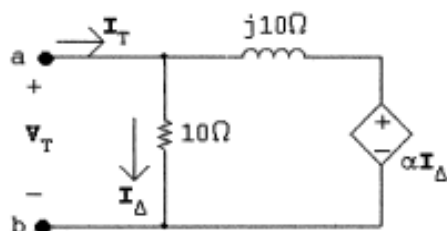

$$I_T = \frac{V_T}{10} + \frac{V_T - \alpha V_T / 10}{j10}$$

$$\frac{I_T}{V_T} = \frac{1}{10} + \frac{(1 - \alpha/10)}{j10} = \frac{(10 - \alpha) + j10}{j100}$$

$$\therefore Z_{Th} = \frac{V_T}{I_T} = \frac{1000 + j100(10 - \alpha)}{(10 - \alpha)^2 + 100}$$

Z_{Th} is real when $\alpha = 10$.

$$[b] Z_{Th} = \frac{1000}{100} = 10 \Omega$$

$$[c] Z_{Th} = 5 + j5$$

$$\frac{1000}{(10 - \alpha)^2 + 100} = 5; \quad (10 - \alpha)^2 = 100$$

$$\therefore 10 - \alpha = \pm 10; \quad \alpha = 10 \mp 10$$



$$\alpha = 0; \quad \alpha = 20$$

But the j term can only equal the real term with $\alpha = 0$. Thus, $\alpha = 0$.

$$[d] Z_{Th} \text{ will be inductive when } \alpha < 10.$$

9.51 Use the node-voltage method to find \mathbf{V}_o in the circuit in Fig. P9.51.

Figure P9.51

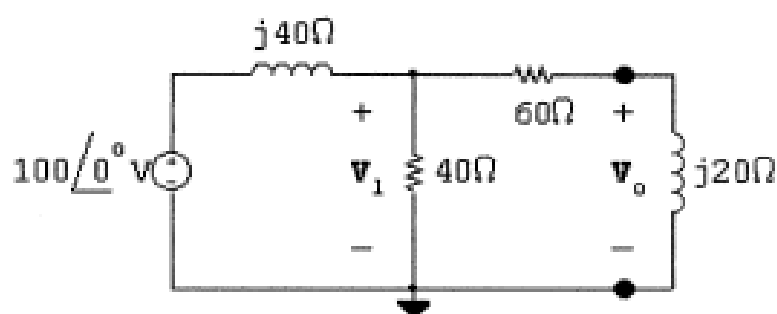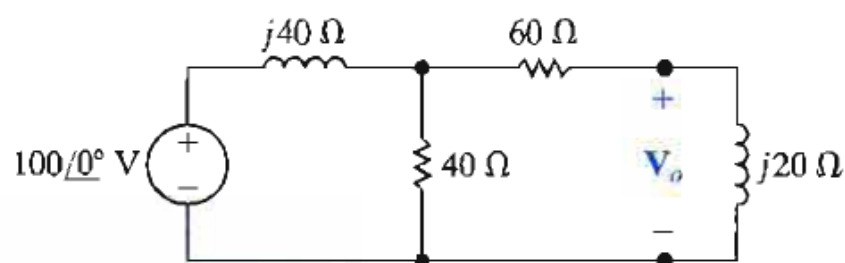

$$\frac{\mathbf{V}_1 - 100}{j40} + \frac{\mathbf{V}_1}{40} + \frac{\mathbf{V}_1}{60 + j20} = 0$$

Solving for \mathbf{V}_1 yields

$$\mathbf{V}_1 = 30 - j40 \text{ V}$$

$$\mathbf{V}_o = \frac{\mathbf{V}_1}{60 + j20}(j20) = \left(\frac{j}{3 + j} \right) \mathbf{V}_1$$


$$\mathbf{V}_o = 15 + j5 \text{ V} = 15.81 \angle 18.43^\circ \text{ V}$$

9.52 Use the node-voltage method to find the steady-state expression for $v_o(t)$ in the circuit in Fig. P9.52 if

$$v_{g1} = 10 \cos(5000t + 53.13^\circ) \text{ V},$$

$$v_{g2} = 8 \sin 5000t \text{ V}.$$

Figure P9.52

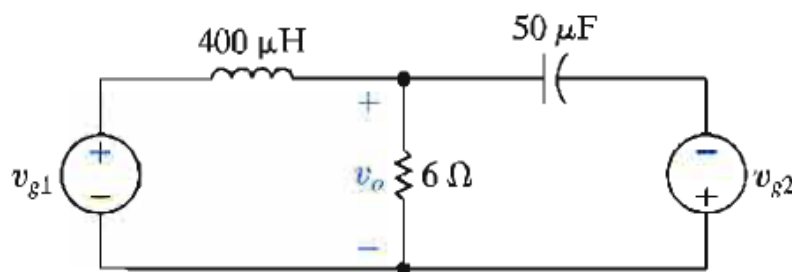


$$j\omega L = j(5000)(0.4 \times 10^{-3}) = j2 \Omega$$

$$\frac{1}{j\omega C} = -j \frac{10^6}{(5000)(50)} = -j4 \Omega$$

$$\mathbf{V}_{g1} = 10 \angle 53.13^\circ = 6 + j8 \text{ V}$$
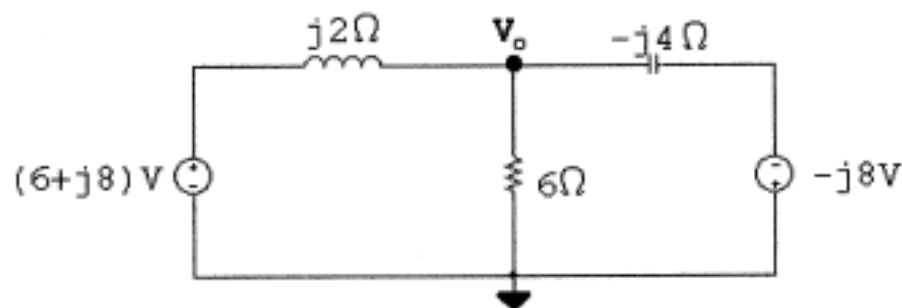
$$\mathbf{V}_{g2} = 8 \angle -90^\circ = -j8 \text{ V}$$



$$\frac{\mathbf{V}_o - 6 - j8}{j2} + \frac{\mathbf{V}_o}{6} + \frac{\mathbf{V}_o + (-j8)}{-j4} = 0$$


Solving,

$$\mathbf{V}_o = 12 \angle 0^\circ$$

$$v_o(t) = 12 \cos 5000t \text{ V}$$

9.53 Use the node voltage method to find the steady-state expressions for the branch currents i_a and i_b in the circuit seen in Fig. P9.53 if $v_a = 100 \sin 10,000t$ V and $v_b = 500 \cos 10,000t$ V.

Figure P9.53

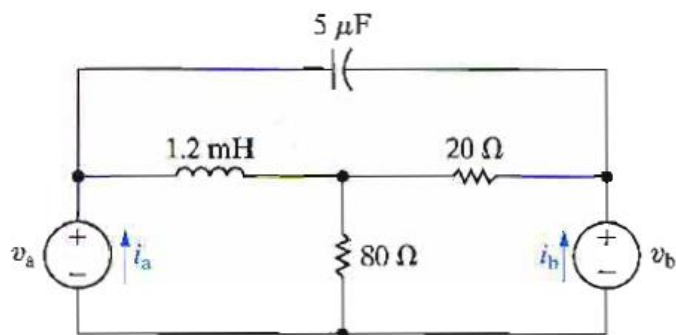


$$j\omega L = j10^4(1.2 \times 10^{-3}) = j12 \Omega$$

$$\frac{1}{j\omega C} = \frac{-j10^6}{5 \times 10^4} = -j20 \Omega$$

$$\mathbf{V}_a = 100/\underline{-90^\circ} = -j100 \text{ V}$$
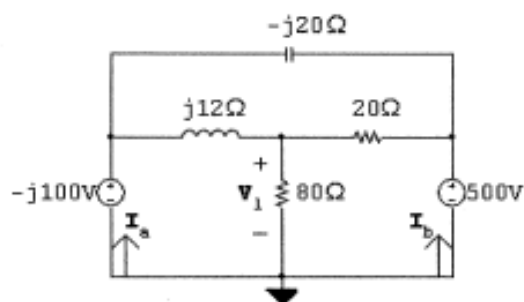
$$\mathbf{V}_b = 500/\underline{0^\circ} = 500 \text{ V}$$



$$\frac{\mathbf{V}_1}{80} + \frac{\mathbf{V}_1 - 500}{20} + \frac{\mathbf{V}_1 + j100}{j12} = 0$$

Solving,

$$\mathbf{V}_1 = 160/\underline{53.13^\circ} \text{ V} = 96 + j128 \text{ V}$$

$$\begin{aligned} \mathbf{I}_a &= \frac{-j100 - 96 - j128}{j12} + \frac{-j100 - 500}{-j20} \\ &= -14 - j17 = 22.02/\underline{-129.47^\circ} \text{ A} \end{aligned}$$



$$i_a = 22.02 \cos(10,000t - 129.47^\circ) \text{ A}$$

$$\begin{aligned} \mathbf{I}_b &= \frac{500 - 96 - j128}{20} + \frac{500 + j100}{-j20} \\ &= 15.2 + j18.6 = 24.02/\underline{50.74^\circ} \text{ A} \end{aligned}$$

$$i_b = 24.02 \cos(10,000t + 50.74^\circ) \text{ A}$$

9.54 Use the node-voltage method to find the phasor voltage \mathbf{V}_g in the circuit shown in Fig. P9.54.

Figure P9.54

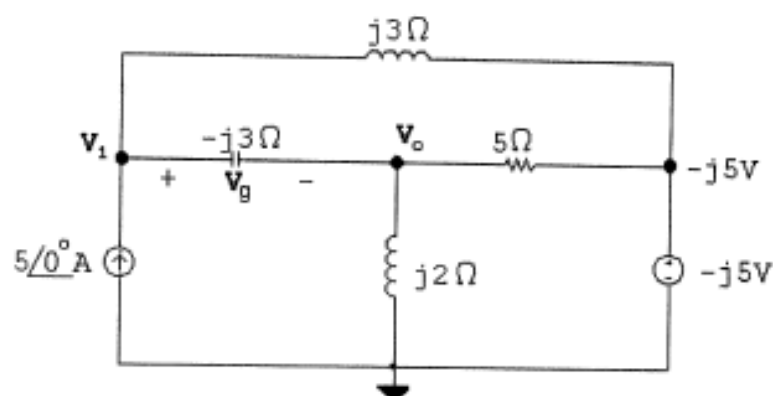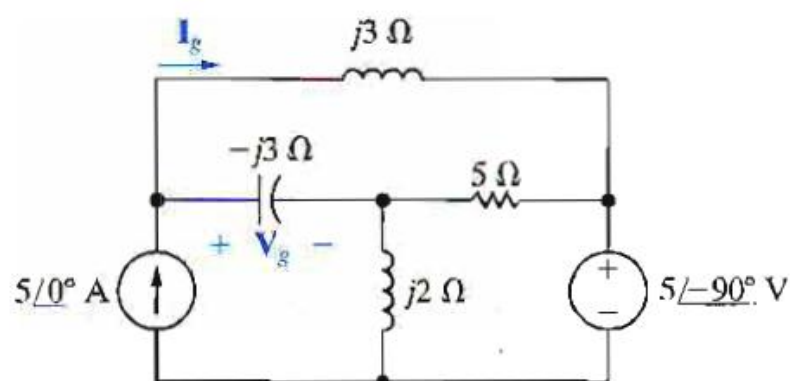

$$\frac{\mathbf{V}_o}{j2} + \frac{\mathbf{V}_o + j5}{5} + \frac{\mathbf{V}_o - \mathbf{V}_1}{-j3} = 0$$

$$(5 + j6)\mathbf{V}_o + 10\mathbf{V}_1 = 30$$



$$-5 + \frac{\mathbf{V}_1 - \mathbf{V}_o}{-j3} + \frac{\mathbf{V}_1 + j5}{j3} = 0$$

$$\mathbf{V}_o = j10; \quad \mathbf{V}_1 = 9 - j5$$

$$\mathbf{V}_g = \mathbf{V}_1 - \mathbf{V}_o = 9 - j5 - j10 = 9 - j15 = 17.49 \angle -59.04^\circ \text{ V}$$

9.55 Use the node-voltage method to find \mathbf{V}_o and \mathbf{I}_o in the circuit seen in Fig. P9.55.

Figure P9.55

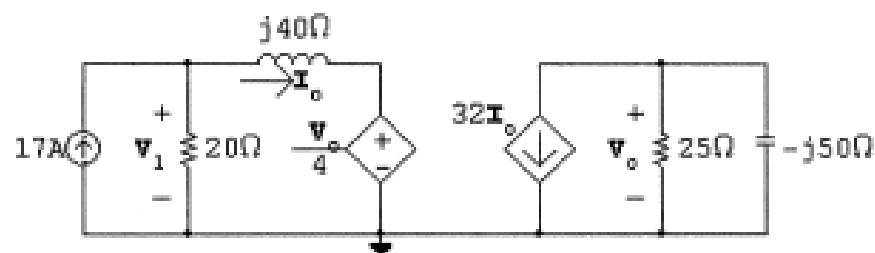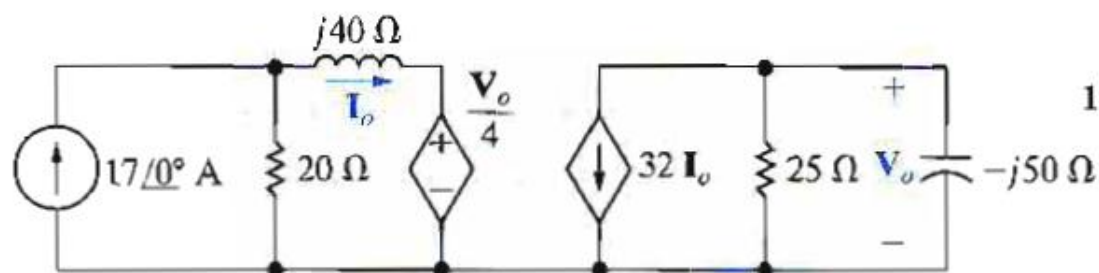

$$\frac{\mathbf{V}_o}{25} + \frac{\mathbf{V}_o}{-j50} + 32\mathbf{I}_o = 0$$

$$(2 + j)\mathbf{V}_o = -1600\mathbf{I}_o$$

$$\mathbf{V}_o = (-640 + j320)\mathbf{I}_o$$

$$\mathbf{I}_o = \frac{\mathbf{V}_1 - (\mathbf{V}_o/4)}{j40}$$

$$\therefore \mathbf{V}_1 = (-160 + j120)\mathbf{I}_o$$


$$17 = \frac{\mathbf{V}_1}{20} + \mathbf{I}_o = (-8 + j6)\mathbf{I}_o + \mathbf{I}_o = (-7 + j6)\mathbf{I}_o$$

$$\therefore \mathbf{I}_o = \frac{17}{(-7 + j6)} = -1.4 - j1.2 \text{ A} = 1.84\angle -139.40^\circ \text{ A}$$

$$\mathbf{V}_o = (-640 + j320)\mathbf{I}_o = 1280 + j320 = 1319.39\angle 14.04^\circ \text{ V}$$

- 9.56** Use the node-voltage method to find the phasor voltage \mathbf{V}_o in the circuit shown in Fig. P9.56. Express the voltage in both polar and rectangular form.

Figure P9.56

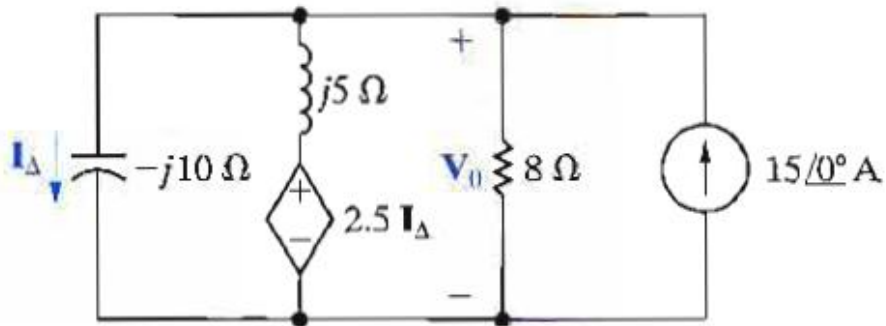

$$-15\angle 0^\circ + \frac{\mathbf{V}_o}{8} + \frac{\mathbf{V}_o - 2.5\mathbf{I}_\Delta}{j5} + \frac{\mathbf{V}_o}{-j10} = 0$$

$$\mathbf{I}_\Delta = \frac{\mathbf{V}_o}{-j10}$$

Solving,


$$\mathbf{V}_o = 72 + j96 = 120\angle 53.13^\circ \text{ V}$$

9.57 Use the mesh-current method to find the steady-state expression for $i_o(t)$ in the circuit in Fig. P9.57 if

$$v_a = 60 \cos 40,000t \text{ V},$$

$$v_b = 90 \sin (40,000t + 180^\circ) \text{ V}.$$


Figure P9.57

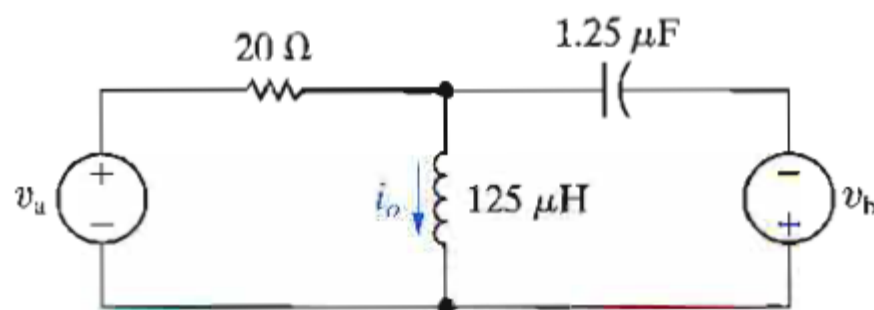

$$\mathbf{V}_a = 60 \angle 0^\circ \text{ V}; \quad \mathbf{V}_b = 90 \angle 90^\circ \text{ V}$$

$$j\omega L = j(4 \times 10^4)(125 \times 10^{-6}) = j5 \Omega$$
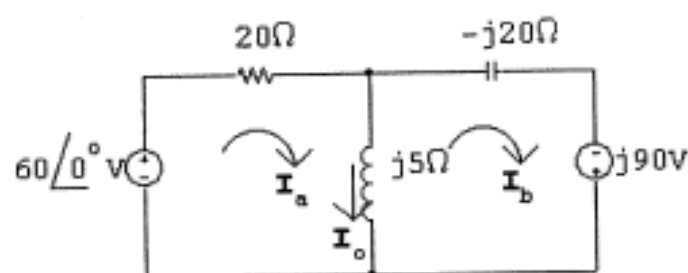
$$\frac{-j}{\omega C} = \frac{-j10^6}{40,000(1.25)} = -j20 \Omega$$



$$60 = (20 + j5)\mathbf{I}_a - j5\mathbf{I}_b$$

$$j90 = -j5\mathbf{I}_a - j15\mathbf{I}_b$$

Solving,


$$\mathbf{I}_a = 2.25 - j2.25 \text{ A}; \quad \mathbf{I}_b = -6.75 + j0.75 \text{ A}$$

$$\mathbf{I}_o = \mathbf{I}_a - \mathbf{I}_b = 9 - j3 = 9.49 \angle -18.43^\circ \text{ A}$$


$$i_o(t) = 9.49 \cos(40,000t - 18.43^\circ) \text{ A}$$

9.58 Use the mesh-current method to find the steady-state expression for $v_o(t)$ in the circuit in Fig. P9.52.

Figure P9.52

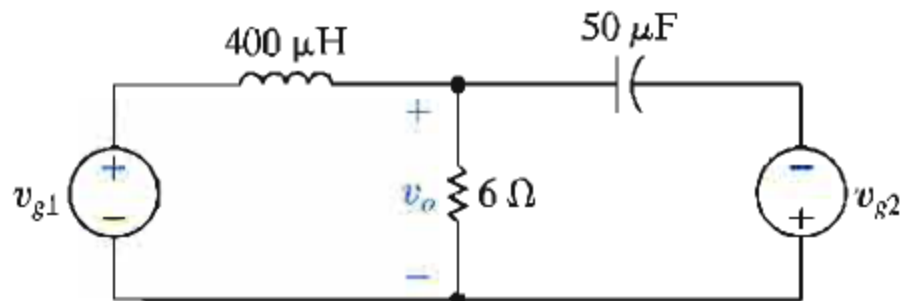

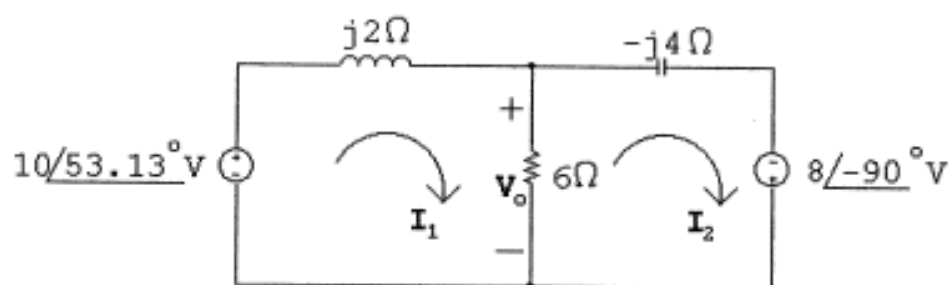From the solution to Problem 9.52 the phasor-domain circuit is



$$10/53.13^\circ = (6 + j2)\mathbf{I}_1 - 6\mathbf{I}_2$$

$$8/-90^\circ = -6\mathbf{I}_1 + (6 - j4)\mathbf{I}_2$$

$$\mathbf{V}_o = (\mathbf{I}_1 - \mathbf{I}_2)6$$



Solving,

$$\mathbf{V}_o = 12/0^\circ \text{ V}$$

$$v_o(t) = 12 \cos 5000t \text{ V}$$

9.59 Use the mesh-current method to find the phasor current \mathbf{I}_g in the circuit in Fig. P9.54.

Figure P9.54

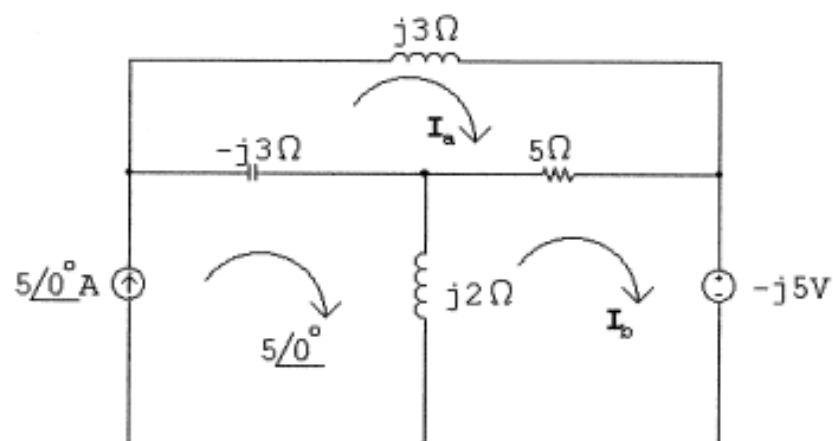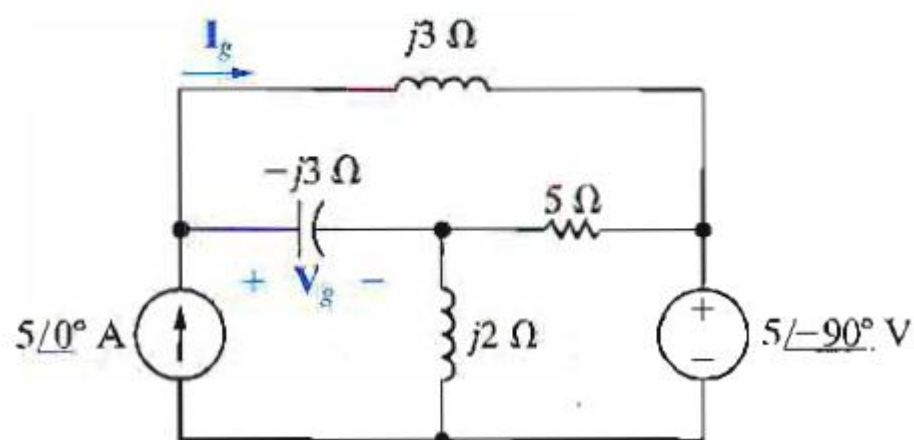

$$j3\mathbf{I}_a + 5(\mathbf{I}_a - \mathbf{I}_b) - j3(\mathbf{I}_a - 5) = 0$$



$$j2(\mathbf{I}_b - 5) + 5(\mathbf{I}_b - \mathbf{I}_a) - j5 = 0$$

Solving,

$$\mathbf{I}_a = -j3; \quad \mathbf{I}_g = -j3 = 3\angle-90^\circ \text{ A}$$

- 9.60 Use the mesh-current method to find the branch currents \mathbf{I}_a , \mathbf{I}_b , \mathbf{I}_c , and \mathbf{I}_d in the circuit shown in Fig. P9.60.

Figure P9.60

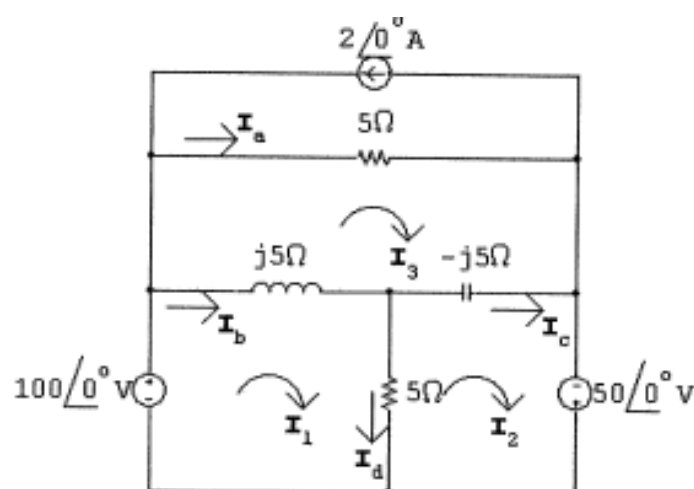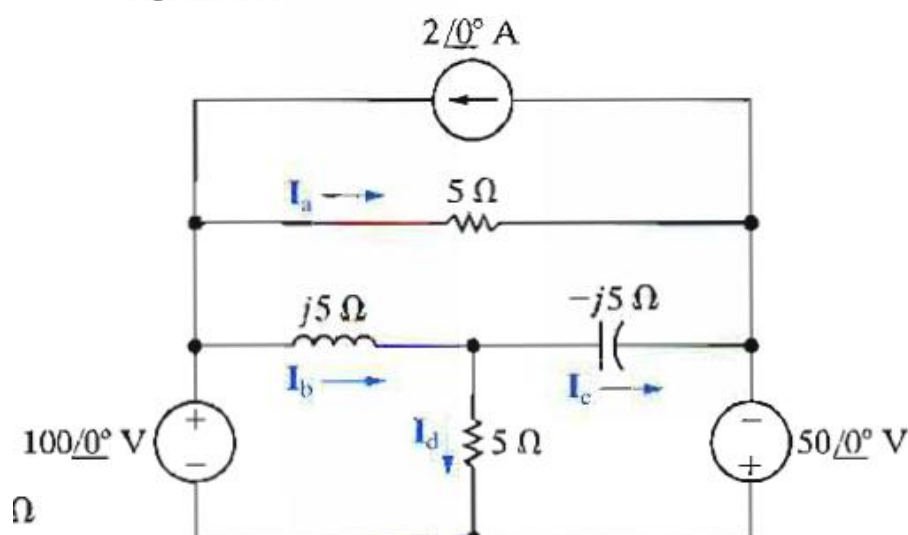

$$100\angle 0^\circ = (5 + j5)\mathbf{I}_1 - 5\mathbf{I}_2 - j5\mathbf{I}_3$$

$$50\angle 0^\circ = -5\mathbf{I}_1 + (5 - j5)\mathbf{I}_2 + j5\mathbf{I}_3$$

$$-10\angle 0^\circ = -j5\mathbf{I}_1 + j5\mathbf{I}_2 + 5\mathbf{I}_3$$

Solving,

$$\mathbf{I}_1 = 58 - j20 \text{ A}; \quad \mathbf{I}_2 = 58 + j10 \text{ A}; \quad \mathbf{I}_3 = 28 + j0 \text{ A}$$

$$\mathbf{I}_a = \mathbf{I}_3 + 2 = 30 + j0 \text{ A}$$

$$\mathbf{I}_b = \mathbf{I}_1 - \mathbf{I}_3 = 58 - j20 - 28 = 30 - j20 \text{ A}$$


$$\mathbf{I}_c = \mathbf{I}_2 - \mathbf{I}_3 = 58 + j10 - 28 = 30 + j10 \text{ A}$$

$$\mathbf{I}_d = \mathbf{I}_1 - \mathbf{I}_2 = 58 - j20 - 58 - j10 = -j30 \text{ A}$$

9.61 Use the mesh-current method to find the steady-state expression for v_o in the circuit seen in Fig. P9.61, if v_g equals $72 \cos 5000t$ V.


PSPICE

Figure P9.61

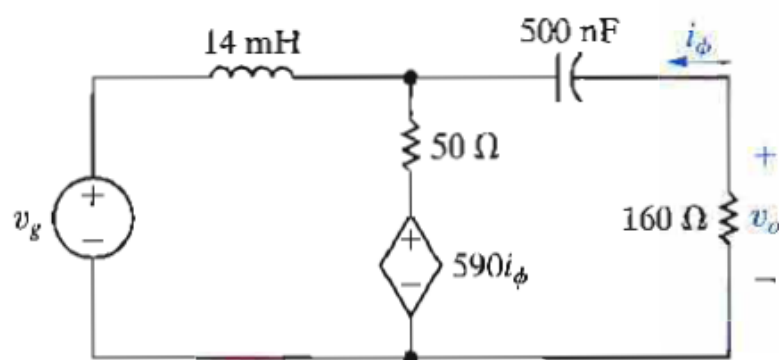

$$j\omega L = j5000(14 \times 10^{-3}) = j70 \Omega$$
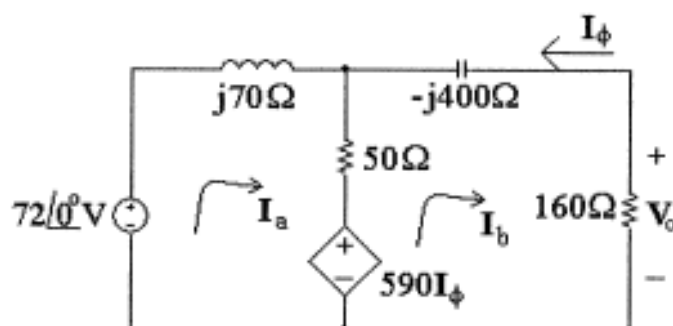
$$\frac{1}{j\omega C} = \frac{-j}{(5000)(0.5 \times 10^{-6})} = -j400 \Omega$$



$$72/0^\circ = (50 + j70)\mathbf{I}_a - 50\mathbf{I}_b + 590(-\mathbf{I}_b)$$

$$0 = -50\mathbf{I}_a - 590(-\mathbf{I}_b) + (210 - j400)\mathbf{I}_b$$

Solving,


$$\mathbf{I}_b = (50 - j50) \text{ mA}$$

$$\mathbf{V}_o = 160\mathbf{I}_b = 8 - j8 = 11.31/-45^\circ$$

$$v_o = 11.31 \cos(5000t - 45^\circ) \text{ V}$$

- 9.62** Use the concept of voltage division to find the steady-state expression for $v_o(t)$ in the circuit in Fig. P9.62 if $v_g = 75 \cos 5000t$ V.

Figure P9.62

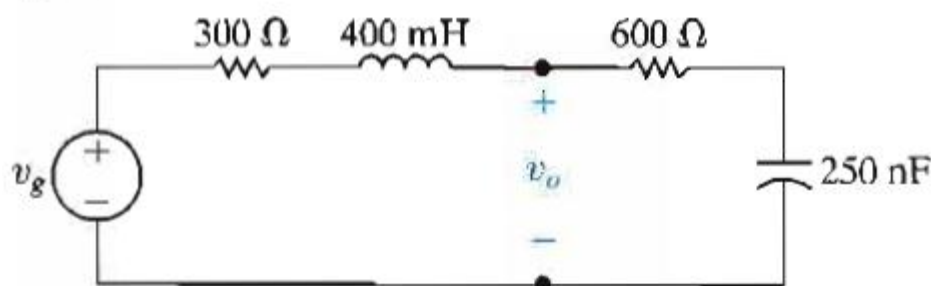

$$Z_o = 600 - j \frac{10^6}{(5000)(0.25)} = 600 - j800\ \Omega$$

$$Z_T = 300 + j2000 + 600 - j800 = 900 + j1200\ \Omega = 1500 \angle 53.13^\circ\ \Omega$$

$$\mathbf{V}_o = \mathbf{V}_g \frac{Z_o}{Z_T} = \frac{(75 \angle 0^\circ)(1000 \angle -53.13^\circ)}{1500 \angle 53.13^\circ} = 50 \angle -106.26^\circ\text{ V}$$

$$v_o = 50 \cos(5000t - 106.26^\circ)\text{ V}$$

- 9.64** The sinusoidal voltage source in the circuit shown in Fig. P9.64 is generating the voltage $v_g = 1.2 \cos 100t$ V. If the op amp is ideal, what is the steady-state expression for $v_o(t)$?

$$\mathbf{V}_g = 1.2 \angle 0^\circ\text{ V}; \quad \frac{1}{j\omega C} = \frac{10^6}{j100} = -j10\text{ k}\Omega$$

Let \mathbf{V}_a = voltage across $1\ \mu\text{F}$ capacitor, positive at upper terminal
Then:

$$\frac{\mathbf{V}_a - 1.2 \angle 0^\circ}{10} + \frac{\mathbf{V}_a}{-j10} + \frac{\mathbf{V}_a}{10} = 0; \quad \therefore \mathbf{V}_a = (0.48 - j0.24)\text{ V}$$

$$\frac{0 - \mathbf{V}_a}{10} + \frac{0 - \mathbf{V}_o}{200} = 0; \quad \mathbf{V}_o = -20\mathbf{V}_a$$

$$\therefore \mathbf{V}_o = -9.6 + j4.8 = 10.73 \angle 153.43^\circ\text{ V}$$

$$v_o = 10.73 \cos(100t + 153.43^\circ)\text{ V}$$